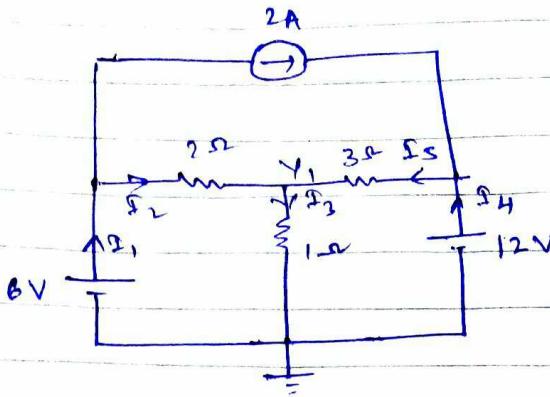


1)



Using Nodal Analysis:

$$I_1 = 2 + I_2 \quad \text{--- (1)}$$

$$\frac{6 - V_1}{2} = I_2 \quad \text{--- (2)}$$

$$\frac{V_1 - 0}{1} = I_3 \quad \text{--- (3)}$$

$$I_5 = I_4 + 2 \quad \text{--- (4)}$$

~~By KCL at node 2~~

$$\frac{12 - V_1}{3} = I_4 \quad \text{--- (5)}$$

$$I_2 + I_5 = I_4 \quad \text{--- (6)}$$

from (1), (2), (3), (5)

$$\left(\frac{6 - V_1}{2}\right) + \left(\frac{12 - V_1}{3}\right) = \left(\frac{V_1 - 0}{1}\right)$$

$$\Rightarrow 3 - \frac{V_1}{2} + 4 - \frac{V_1}{3} = V_1$$


$$\Rightarrow 7 = V_1 \left[1 + \frac{1}{2} + \frac{1}{3} \right]$$

$$\Rightarrow V_1 = \frac{6 \times 7}{11} = 3.81 \text{ V}$$

$$I_2 = \frac{6 - 3.81}{2} = 1.09 \text{ A} \quad \text{--- (7)}$$

$$I_3 = \frac{V_1 - 0}{1} = 3.81 \text{ A}$$
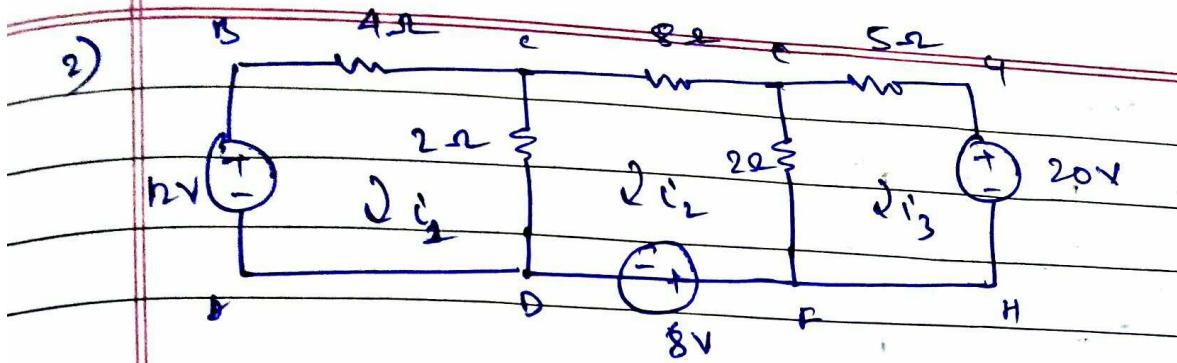
$$I_5 = \frac{12 - V_1}{3} = 2.72 \text{ A}$$



Σ_n ABCD

$$12 - 4i_1 - 2(i_1 - i_2) = 0 \\ \Rightarrow 12 = 6i_1 - 2i_2 \quad \text{--- (1)}$$

Σ_n DCEF

$$-8 - 2(i_2 - i_1) - 8i_2 - 2(i_2 - i_3) = 0 \\ \Rightarrow -8 - 12i_2 + 2i_1 + 2i_3 = 0 \\ \Rightarrow -12i_2 + 2i_1 + 2i_3 = 8 \quad \text{--- (2)}$$

Σ_n FEGH

$$-20 - 2(i_3 - i_2) - 5i_3 = 0 \\ -20 - 7i_3 + 2i_2 = 0 \\ 2i_2 - 7i_3 = 20 \quad \text{--- (3)}$$

$$\frac{i_1}{i_2} = K.T.H.D.Y$$


Solving (1), (2) & (3).

$$i_1 = 1.7A$$


$$i_2 = -0.9A$$

$$i_3 = -3.11A$$
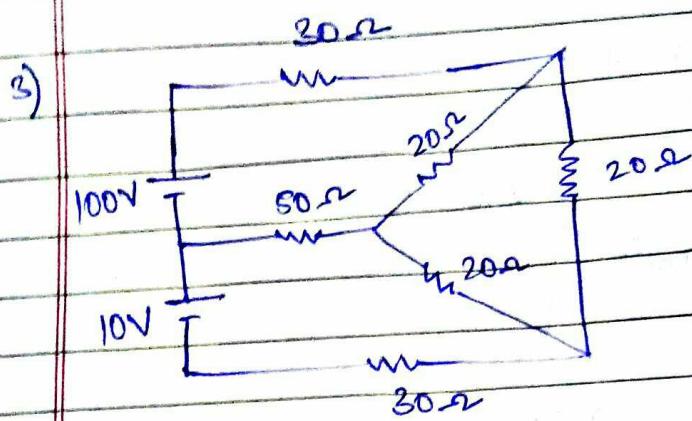
$$P_{8\Omega} = i^2 R \\ = (0.9)^2 \cdot 8 \\ = 6.48W$$



On Source transformation

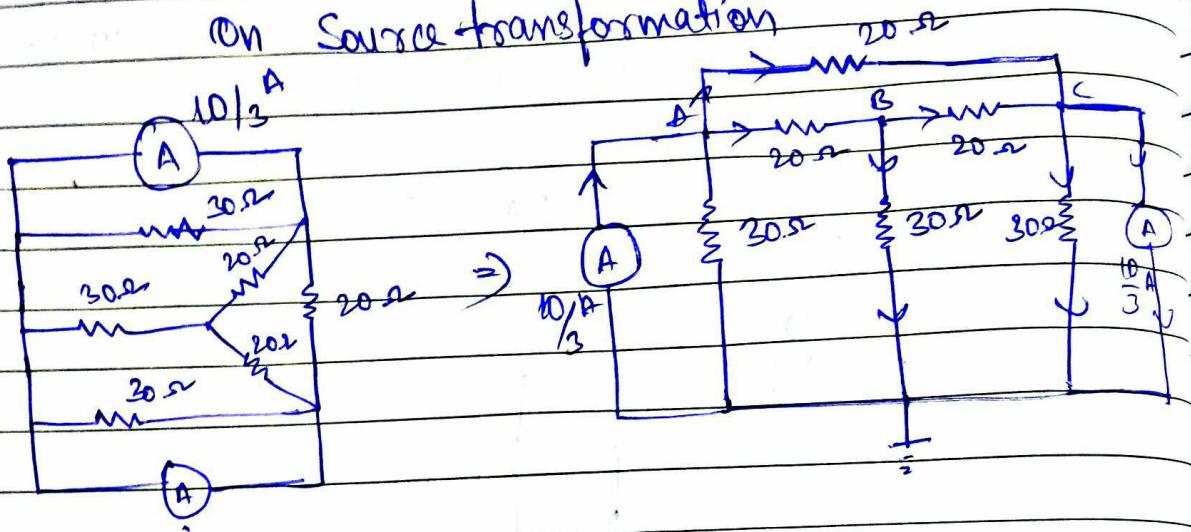

Using Nodal Analysis

Node A

$$\frac{10}{3} = \frac{V_A}{30} + \frac{V_A - V_B}{20} + \frac{V_A - V_C}{20}$$

$$\Rightarrow \frac{100}{3} = \frac{V_A}{3} + \frac{V_A - V_B}{2} + \frac{V_A - V_C}{2}$$

$$\Rightarrow \frac{100}{3} = \frac{2V_A + bV_B - 3V_C}{\beta_2}$$

$$3) 200 = 8V_A - 3V_B - 3V_C$$

$$\boxed{8V_A - 3V_B - 3V_C = 200} \quad (i)$$

Node B

$$\frac{V_A - V_B}{20} = \frac{V_B - 0}{30} + \frac{V_B - V_C}{20}$$

$$\frac{V_A - V_B}{2} = 2V_B + 3V_B - 3V_C$$

$$\Rightarrow [3V_A - 8V_B + 3V_C = 0] \quad -(ii)$$

Node C

$$\frac{V_B - V_C}{20} + \frac{V_A - V_C}{20} = \frac{V_C + 10}{30} + \frac{10}{3}$$

$$\Rightarrow \frac{V_B - V_C}{2} + \frac{V_A - V_C}{2} - \frac{V_C}{3} = \frac{10}{3}$$

$$\Rightarrow \frac{3V_B - 3V_C + 3V_A - 3V_C - 2V_C}{2} = \frac{10}{3}$$

$$\Rightarrow [3V_B + 3V_A - 8V_C = 20] \quad -(iii)$$

Using calculator

$$V_A = 18.18V$$

$$V_B = 0V$$

$$V_C = -18.18V$$


$$V_{CD} = V_A - V_C = 18.18 - (-18.18) = 36.36V$$

~~$$I = \frac{V_{CD}}{R} = \frac{36.36}{20} A$$~~

$$I = \frac{V_{CD}}{R} = \frac{36.36}{20} = 1.818A$$

$$V_{CD} = 36.36V$$

$$I = 1.818A$$

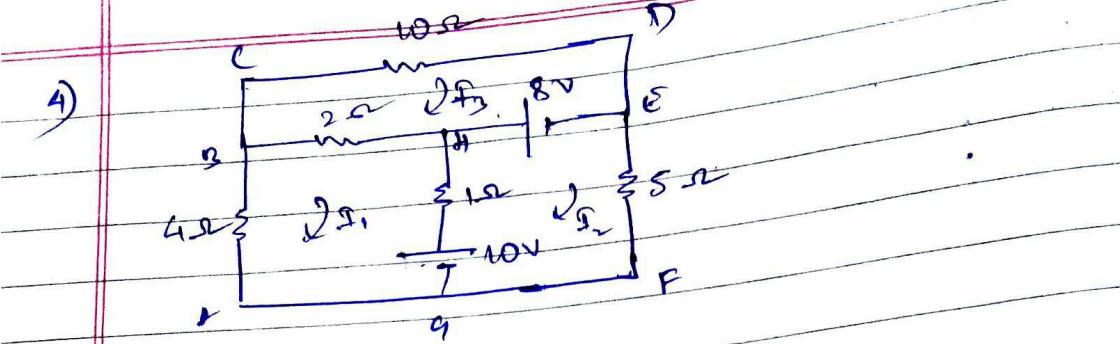

2n ABHG

$$-4I_1 - 2(I_1 - I_2) - 1(I_1 - I_2) - 10 = 0 \quad (1)$$

$$-7I_1 + I_2 + 2I_2 = 10$$

2n GHFR

$$10 - 1(I_2 - I_1) - 8 - 5I_2 = 0$$

$$I_1 - 6I_2 = -2 \quad (II)$$

2n BCDE

$$-10I_3 + 8 - 2(I_3 - I_1) = 0$$

$$2I_1 - 12I_3 = -8 \quad (III)$$

Solving (1), (II) & (III)

$$I_1 = -1.28 \text{ A}$$

$$I_2 = 0.12 \text{ A}$$

$$I_3 = 0.45 \text{ A}$$

$$I = I_2 - I_1$$

$$= 0.12 + 1.28$$

$$I = 1.4 \text{ A} \quad \Leftarrow \text{Ans.}$$

$$5) \frac{x_L - x_C}{R} = \tan \phi$$

$$\omega = 314 \text{ rad/s}$$

$$x_C = \frac{1}{\omega C} = 63.7 \Omega$$

$$z^2 = R^2 + (x_L - x_C)^2 \quad -(i)$$

$$\tan 30^\circ = \frac{x_L - x_C}{R}$$

$$\frac{1}{\sqrt{3}} = x_L - x_C \quad -(ii)$$

$$\text{Now: } z^2 = R^2 + \frac{R^2}{3} \quad \text{from (i) \& (ii)}$$

$$z^2 = \frac{4R^2}{3} \quad (iii)$$

$$z = \frac{V_m}{I_m} = \frac{230}{2} = 115 \quad -(iv)$$

From (ii) & (iv)

$$(115)^2 = \frac{4R^2}{3}$$


$$R = 99.59 \Omega \approx 99.6 \Omega$$

$$x_L = x_C + \frac{R}{\sqrt{3}} = 63.7 + 57.5 = 121.2$$


$$L = \frac{121.2}{314} = 0.386 H$$

$$\begin{aligned}
 \text{(ii)} \quad N_{coil} &= I \cdot X_L \\
 &= \left(2 \times \frac{\sqrt{3}}{2} + \frac{2}{2} j \right) \cdot (0.386 j) \\
 &= 0.386 + 0.669 j \\
 &= 0.77 \angle 315^\circ V
 \end{aligned}$$

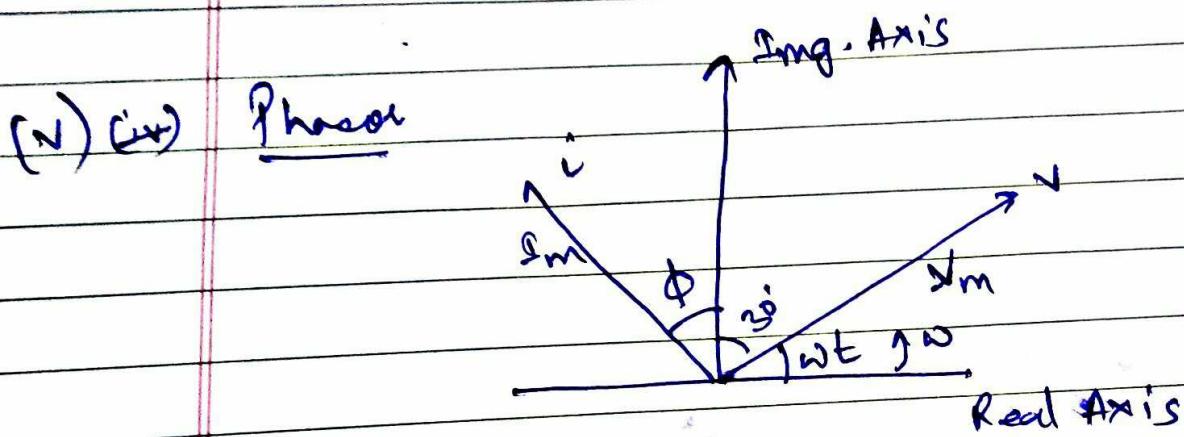
$$\begin{aligned}
 \text{(iii)} \quad N_c &= I \cdot X_C \\
 &= (\sqrt{3} + j) (-50\mu j) \\
 &= -50\mu - 50\sqrt{3}\mu \\
 &= 50 \times 4 \mu \angle -60^\circ \\
 &= 200 \times 10^{-6} \angle -60^\circ \\
 V_C &= 0.2 \times 10^{-3} \angle -60^\circ V
 \end{aligned}
 \quad \text{(iv)} \quad \phi = 30^\circ$$



phase - Difference

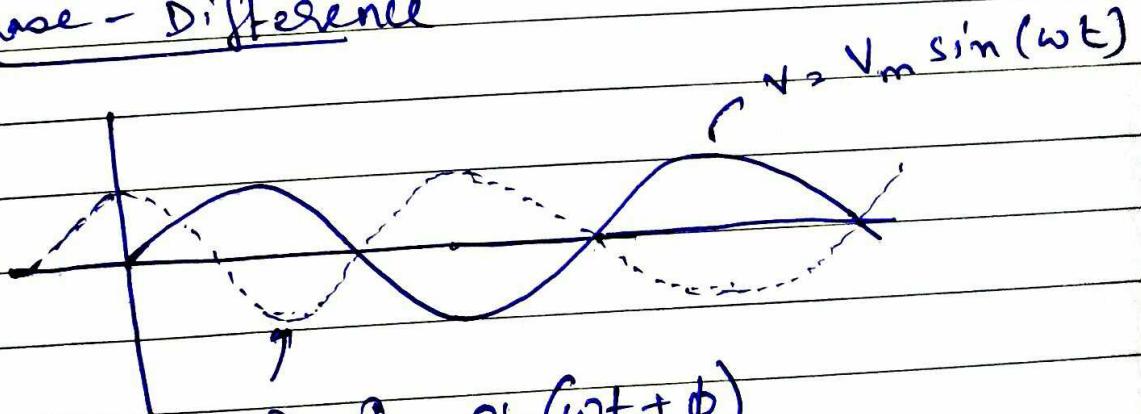

$$67) \omega = 50 \text{ rad/sec}$$


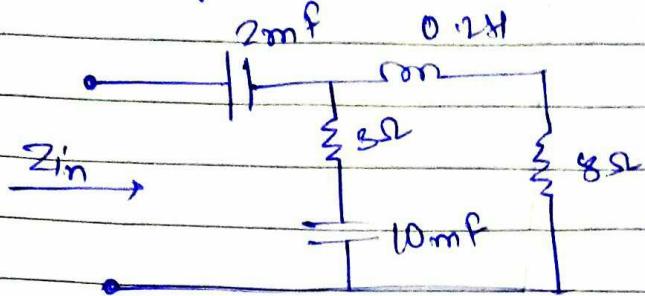


$$X_L = \omega L = 50 \times 0.2 = 10 \Omega$$

$$X_C_1 = \frac{1}{\omega C} = \frac{1}{50 \times 10 \times 10^{-3}} = \frac{1}{100 \times 10^{-3}} = 10 \Omega$$

$$X_C_2 = \frac{1}{\omega C} = \frac{1}{50 \times 2 \times 10^{-3}} = \frac{10}{5} = 2 \Omega$$

~~parallel~~

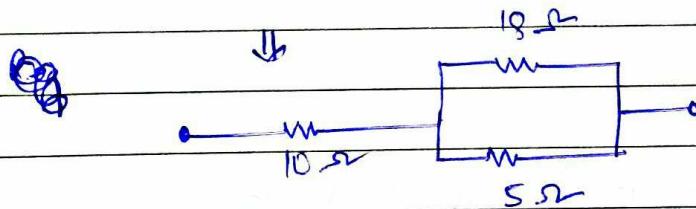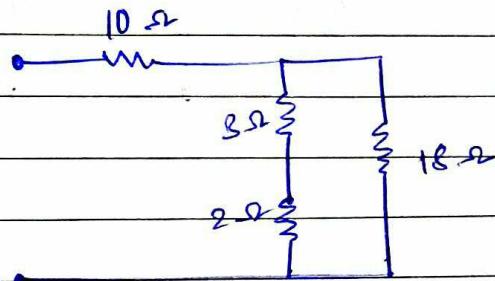


$$R_{eq} = (18 \parallel 5) + 10$$

$$= \frac{18 \times 5}{23} + 10$$

$$= \frac{90}{23} + 10$$

$$= \frac{90 + 230}{23} = \frac{320}{23} = 13.91 \Omega$$

$$\therefore Z_{in} = 13.91 \Omega$$

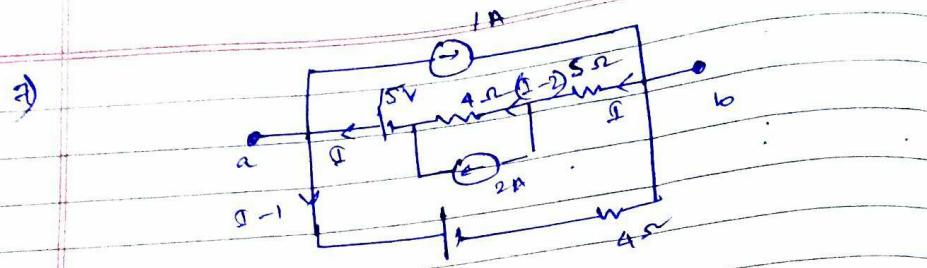

KVL, KCL

$$15 - 8 - 4(\underline{I} - 1) - 5\underline{I} - 4(\underline{I} - 2) = 0$$

$$\Rightarrow 15 - 8 + 4 + 8 - 13\underline{I} = 0$$

$$\Rightarrow 13\underline{I} = 19$$


$$\Rightarrow \underline{I} = \frac{19}{13}$$

$$V_{ab} = -8 - 4\left(\frac{19}{13} - 1\right)$$

$$= -8 - \frac{4 \times 6}{13}$$

$$V_{ab} = -9.85V \quad [V_a - V_b]$$



for R-eq.

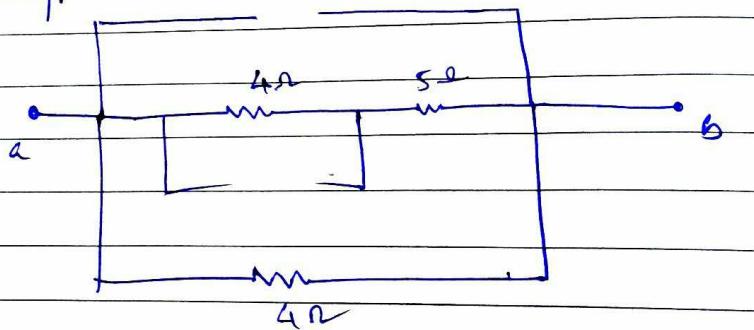


$$R_{ab} = (4+5) // 4$$

$$= \frac{9 \times 4}{13} = \frac{36}{13} = 2.76\Omega$$

Eq. circuit:

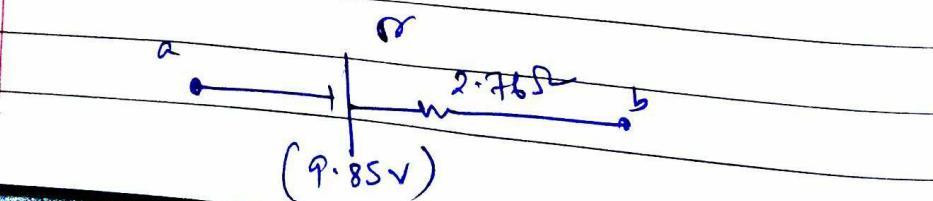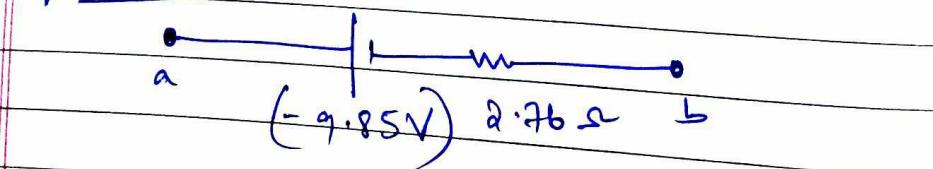

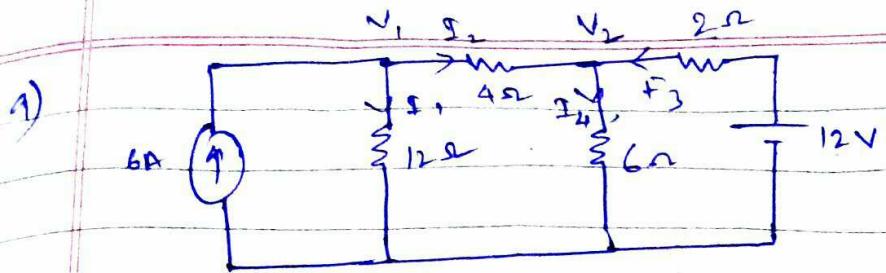

At V₁

$$\frac{V_1 - 0}{12} = I_1$$

$$\frac{V_1 - V_2}{4} = I_2$$

$$6 = I_1 + I_2$$

$$\Rightarrow 6 = \frac{V_1}{12} + \frac{V_1 - V_2}{4}$$

$$\Rightarrow 6 = V_1 \left[\frac{1}{12} + \frac{1}{4} \right] - \frac{V_2}{4}$$

$$\Rightarrow 6 = \frac{V_1}{3} - \frac{V_2}{4} \quad -\textcircled{1}$$

At V₂

$$\frac{V_2 - 0}{6} = I_4$$

$$\frac{12 - V_2}{2} = I_3$$

$$I_2 + I_3 = I_4$$

$$\frac{V_1 - V_2}{4} + \frac{12 - V_2}{2} = \frac{V_2}{6}$$

$$\frac{V_1}{4} + V_2 \left(-\frac{1}{4} - \frac{1}{2} - \frac{1}{6} \right) = -6$$

$$\frac{V_1}{4} + V_2 \left(-\frac{11}{12} \right) = -6 \quad \textcircled{2}$$

From \textcircled{1} & \textcircled{2}

$$V_1 = 28.8$$


$$V_2 = 14.4$$

$$I_1 = \frac{V_1 - 0}{12} = \frac{28.8}{12} = 2.4 \text{ A}$$

$$I_2 = \frac{28.8 - 14.4}{4} = 3.6 \text{ A}$$

$$I_3 = \frac{12 - 14.4}{2} = -1.2 \text{ A}$$

$$I_4 = \frac{14.4}{6} = 2.4 \text{ A}$$

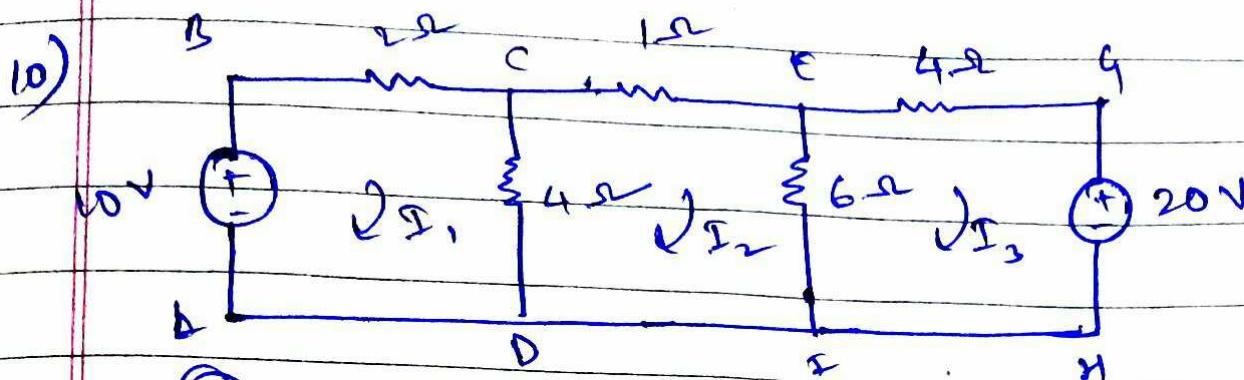

(A) Mesh

In ABCD

$$10 - 2I_1 - 4(I_1 - I_2) = 0$$

$$10 = 6I_1 - 4I_2 \quad \textcircled{1}$$

In DCEF

$$-4(I_2 - I_1) - I_2 - 6I_2 + 6I_3 = 0$$

$$\Rightarrow +4I_1 - 11I_2 + 6I_3 = 0 \quad \textcircled{ii}$$

In EFGH

$$-4I_3 - 20 - 6(I_3 - I_2) = 0$$


$$\Rightarrow -6I_2 - 10I_3 = 20 \quad \textcircled{iii}$$

From ①, ii & iii

$$I_1 = 0.92 \text{ A}$$

$$I_2 = -1.13 \text{ A}$$

$$I_3 = -2.68 \text{ A}$$

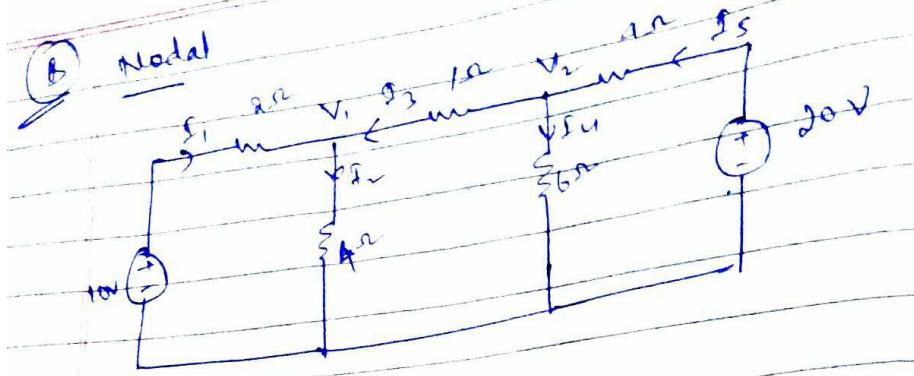

$$\frac{10 - V_1}{2} = I_1 \quad \frac{20 - V_2}{4} = I_5$$

$$\frac{V_1 - 0}{4} = I_2 \quad \frac{V_2 - 0}{6} = I_4$$

$$\frac{V_2 - V_1}{1} = I_3$$

$$I_1 + I_3 = I_2$$

$$I_5 = I_4 + I_3$$

$$\Rightarrow \frac{10 - V_1}{2} + \frac{V_2 - V_1}{1} = \frac{V_1 - 0}{4}$$

$$\frac{20 - V_2}{4} = \frac{V_2 - 0}{6} + \frac{V_2 - V_1}{1}$$

$$\Rightarrow S = V_1 \left[\frac{1}{4} + \frac{1}{2} + 1 \right] - V_2$$

$$\Rightarrow S = -V_1 + V_2 \left(\frac{1}{6} + 1 + \frac{1}{4} \right)$$

$$\Rightarrow S = \frac{7V_1}{4} - V_2 \quad \textcircled{1}$$

$$\Rightarrow S = -V_1 + \frac{17}{12} V_2 \quad \textcircled{11}$$

From ① & ⑪

$$V_1 = 8.17V$$

$$V_2 = 9.29V$$

$$I_1 = \frac{10 - V_1}{2} = 0.92A$$

②

$$I_2 = \frac{V_1}{4} = 2.05A$$

$$I_5 = \frac{20 - V_2}{4} = 2.67A$$

$$I_3 = \frac{V_2 - V_1}{1} = 1.12A$$

$$I_4 = \frac{V_2 - 0}{6} = 1.54A$$

$$(i) R = 1000 \Omega$$

$$L = 100 \text{ mH} = 100 \times 10^{-3} \text{ H}$$

$$C = 10 \text{ pF} = 10 \times 10^{-12} \text{ F}$$

$$N = 100 \text{ V}$$

$$(i) \omega_2 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-1} \times 10^{-11}}} \text{ rad/s}$$

$$\omega = 10^6$$

$$f_2 = \frac{\omega}{2\pi} = \frac{10^6}{2\pi}$$

$\therefore f_2 = 159159 \text{ Hz}$

$$\therefore f = 159159 \text{ sec}^{-1}$$

$$(ii) Q = \frac{X_C}{R} = \frac{X_L}{R}$$

$$= \frac{\omega L}{R}$$

$$= \frac{10^6 \times 100 \times 10^{-3}}{1000}$$

$$Q = 100$$

$$(iii) P = \frac{P_{\max}}{2}$$

$$\frac{V^2}{2} \cos \phi = \left(\frac{V^2}{2}\right) \frac{1}{2}$$

$$\cos \phi = \frac{1}{2} \Rightarrow \phi = 60^\circ$$

$$\tan \phi = \frac{X_L - X_C}{R} = \tan 60^\circ$$

$$X_L - X_C : \frac{\sqrt{3}}{R}$$

$$X_L - X_C = \sqrt{3} R$$

$$\omega \times 100 \times 10^{-2} - \frac{1}{\omega 10^{-11}} = \sqrt{3} \times 1000$$

$$\Rightarrow \omega^2 10^{12} - 1 = \sqrt{3} \omega 10^{-8}$$

$$\Rightarrow \omega^2 10^{-3} - (\sqrt{3} \times 10^{-8}) - 1 = 0$$

$$\Rightarrow \omega = 31.6$$

$$f = \frac{\omega}{2\pi} = \frac{31.6}{2 \times 3.14} = 5 \text{ sec}^{-1}$$

————— x —————

11.7) Band width = $\frac{f_c}{Q} = \frac{159155}{100} = 1591.55 \text{ Hz}$

n) a) $\omega = 314$
 $X_C \cdot \frac{1}{\omega C} = \frac{10^4}{314 \times 80} = 39.8$

$$Z = \sqrt{R^2 + (X_C)^2}$$

$$= \sqrt{(25)^2 + (39.8)^2}$$

$$Z = 47.52$$

$$I_m = \frac{V}{Z} = \frac{100}{47.52} = 2.13 A$$



$$\tan \theta = \frac{X_C}{R}$$

$$\theta = 58^\circ$$

$$i = i_m \sin(\omega t + \theta)$$

$$= 2.13 \sin(314t + 58^\circ)$$

b) $P = \frac{1}{2} V I \cos \phi = \frac{1}{2} \times 100 \times 2.13 \times \cos 58^\circ = 56.4 W$

c) In RC circuit:

$$i = i_0 e^{-t/RC}$$

$$\Rightarrow i = \frac{i_0}{2} \text{ at } t$$

$$\Rightarrow \frac{i_0}{2} = i_0 e^{-t/RC}$$

$$\Rightarrow \frac{1}{2} = e^{-t/RC}$$

$$\Rightarrow \ln 2 \cdot RC = t \Rightarrow t = 1.4 \times 10^{-3} \text{ sec}$$

charge in circuit:

$$q_1 = CV(1 - e^{-t/RC}) \\ = 80 \times 10^{-6} \times 100 (1 - 1/e)$$

$$= \frac{80 \times 100 \times 10^{-6}}{2}$$

$$q_1 = 4 \times 10^{-3} C$$

Voltage across $C = \frac{q_1}{C}$

$$= \frac{4 \times 10^{-3}}{80 \times 10^{-6}} = 50 V$$