

Verification of NETWORK THEOREMS

(Maximum Power Transfer Theorem)


Aim: To verify the maximum power transfer theorem for the given network by theoretical values and simulation values

Apparatus/Tool required:

ORCAD / Capture CIS --> Analog Library - R,
Source Library - Vdc, Idc &
Ground (GND) - 0 (zero)



Simulation Settings: Analysis Type - Bias Point

Circuit Diagram

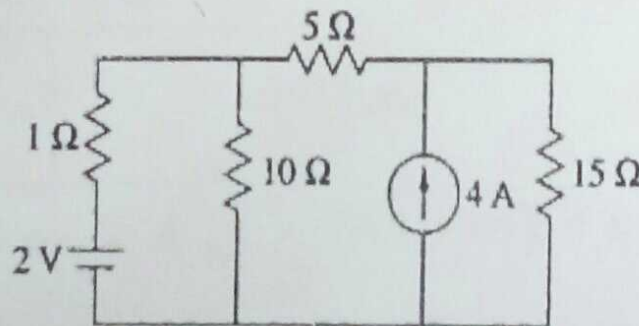

Statement: Maximum Power Transfer Theorem

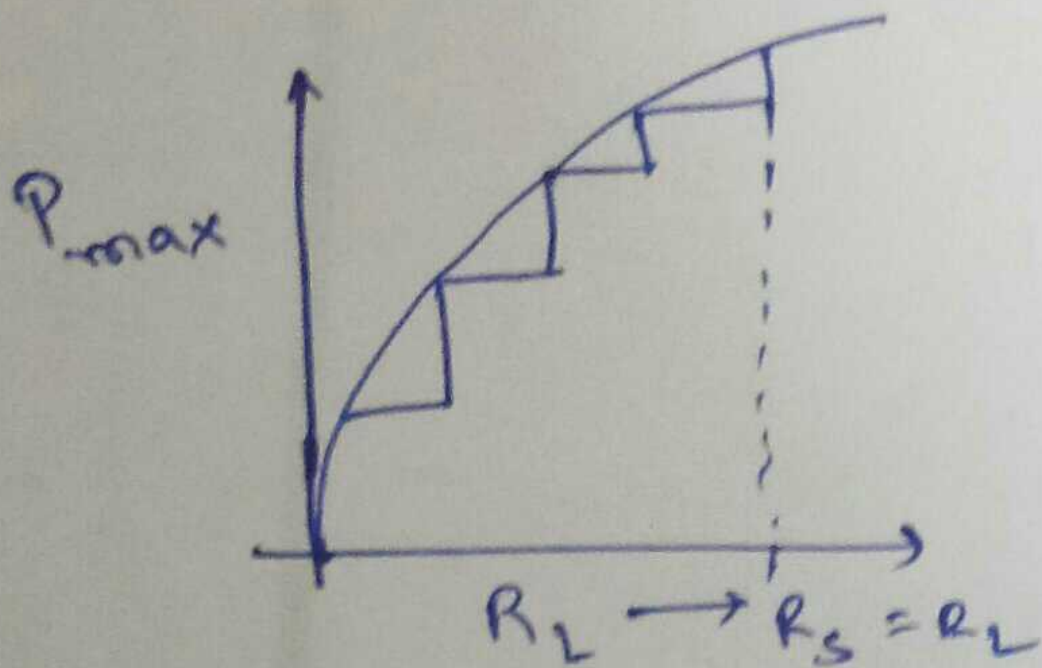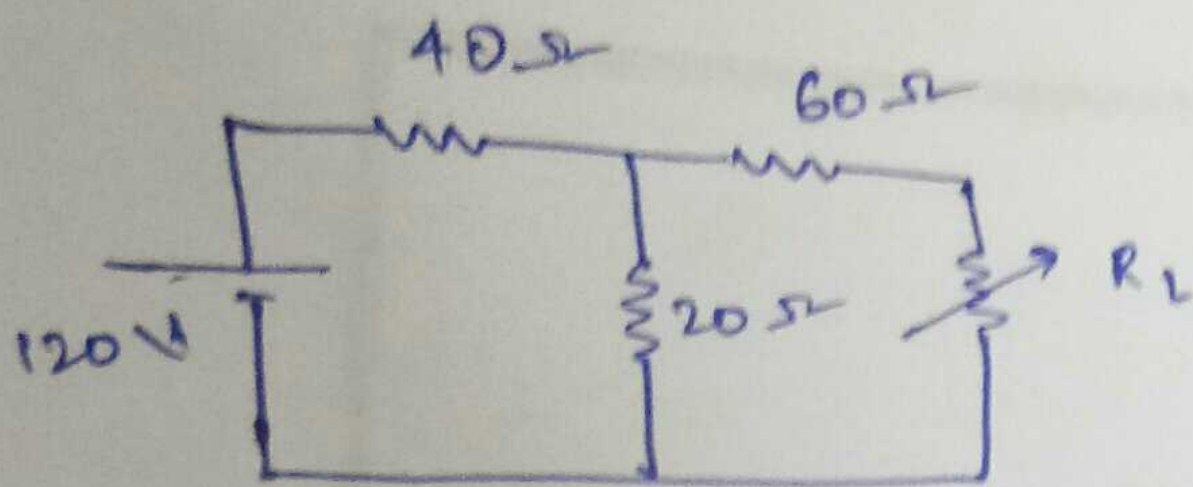
In a linear bilateral network, the maximum power is transferred from source to the load resistance, when the source resistance is equal to load resistance.



$$(R_L = R_{Th})$$

Manual Calculations:


To Find V_{oc} :

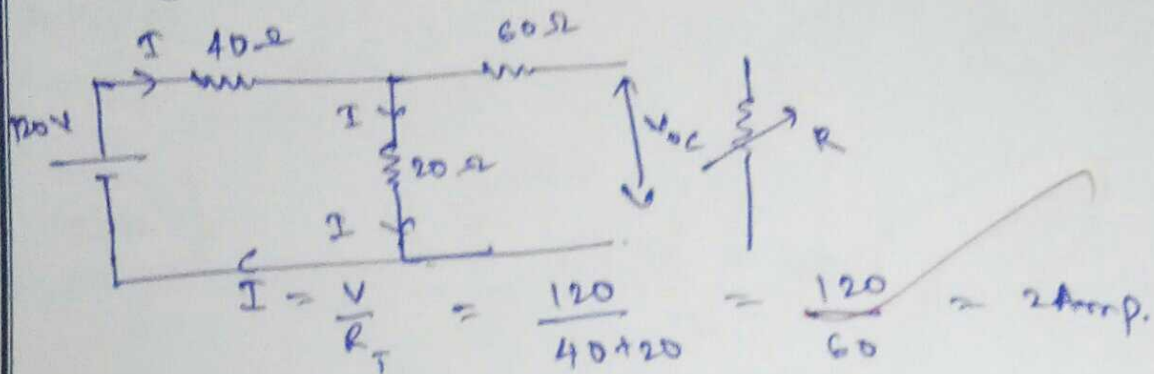

$$V_{20\Omega} = I_{20\Omega} \times R_{20\Omega} = 2 \times 20 = 40 \text{ V}$$

$$V_{oc} = V_{Th} = \boxed{40 \text{ V}}$$

To Find R_{Th} :

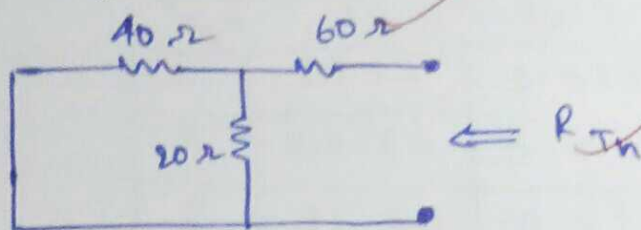


$$R_{AB} = R_i = R_{Th} = (40 \parallel 20) + 60$$

$$= \frac{40 \times 20}{40+20} + 60 = \frac{800}{60} + 60$$

$$R_L = R_{Th} = \boxed{73.33 \Omega}$$

$$= 72.33 \Omega$$

To Find Power:

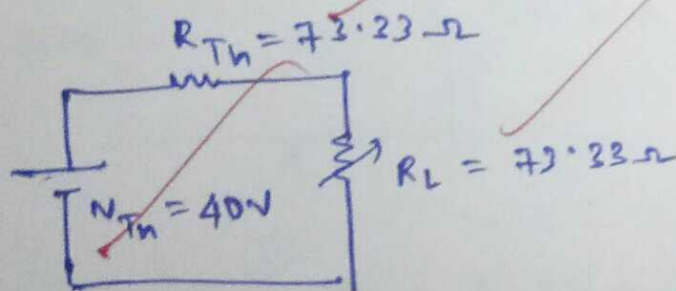

$$I = \frac{V_{Th}}{R_{Th} + R_L} = \frac{40}{73.33 + 73.33}$$

$$I_L = 0.27 \text{ A}$$


$$P_L = I_L^2 R_L = (0.27)^2 \times 73.33$$

8

$$\boxed{P_L = 5.45 \text{ W}}$$

Simulation Circuit:


To Find V_{th} :

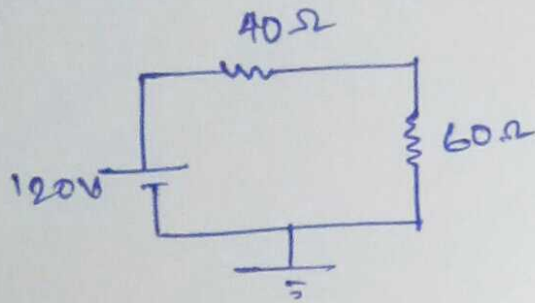

$$V_L = 40V$$


To Find R_{th} :

V_L	I (mA)	R (kΩ)
2	27.27	0.0733
4	54.55	0.0733
6	81.82	0.0733

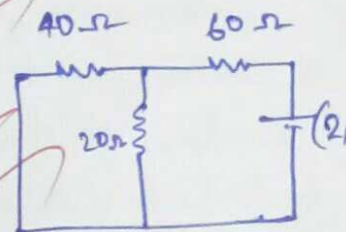

$$(R_{Th})_{Avg} = 0.0733 k\Omega$$

To Find Power:

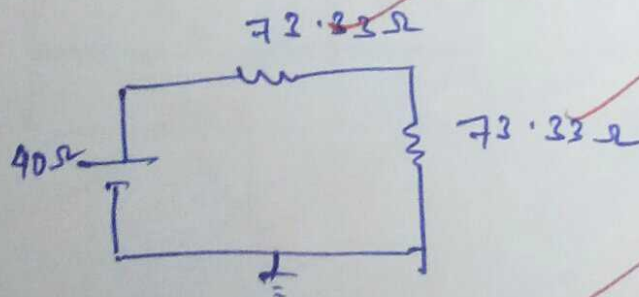

$$I_L = 0.27 mA$$


$$P = 5.45 W$$

The maximum power transfer theorem have been verified for the given network by theoretical and simulation values and the following results are tabulated

Parameters	Theory	Simulation
Result: V_{Th}	40 V	40 V
R_{Th}	73.33 Ω	73.33 Ω
Manual Calculations	<div>Maximum Power Transfer Theorem</div> <div>Simulated Result</div>	
I_L	0.27 A	0.27 A
P_{max}	5.45 W	5.45 W

Inference:

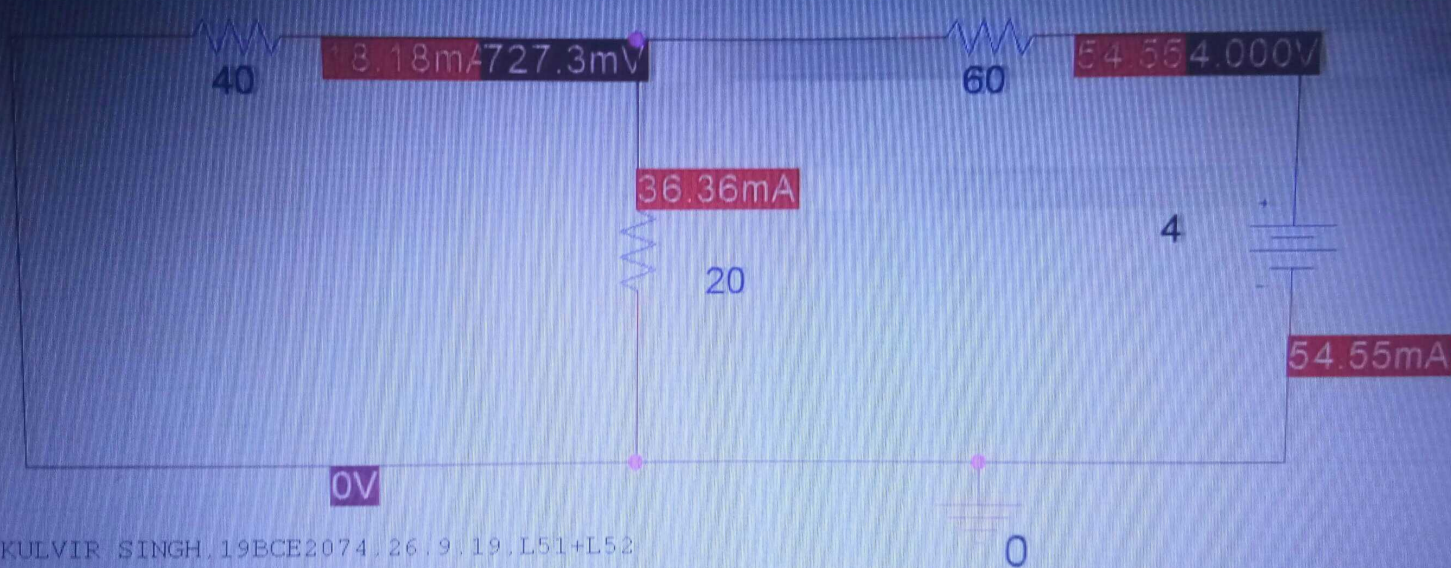Reg. No: 19BCE2074 Name: Kulvir Singh Date: 26/09/19




KULVIR SINGH.19BCE2074.26.9.19.L51+L52

0

1 item selected


1164 x 873px

Size: 134.7KB

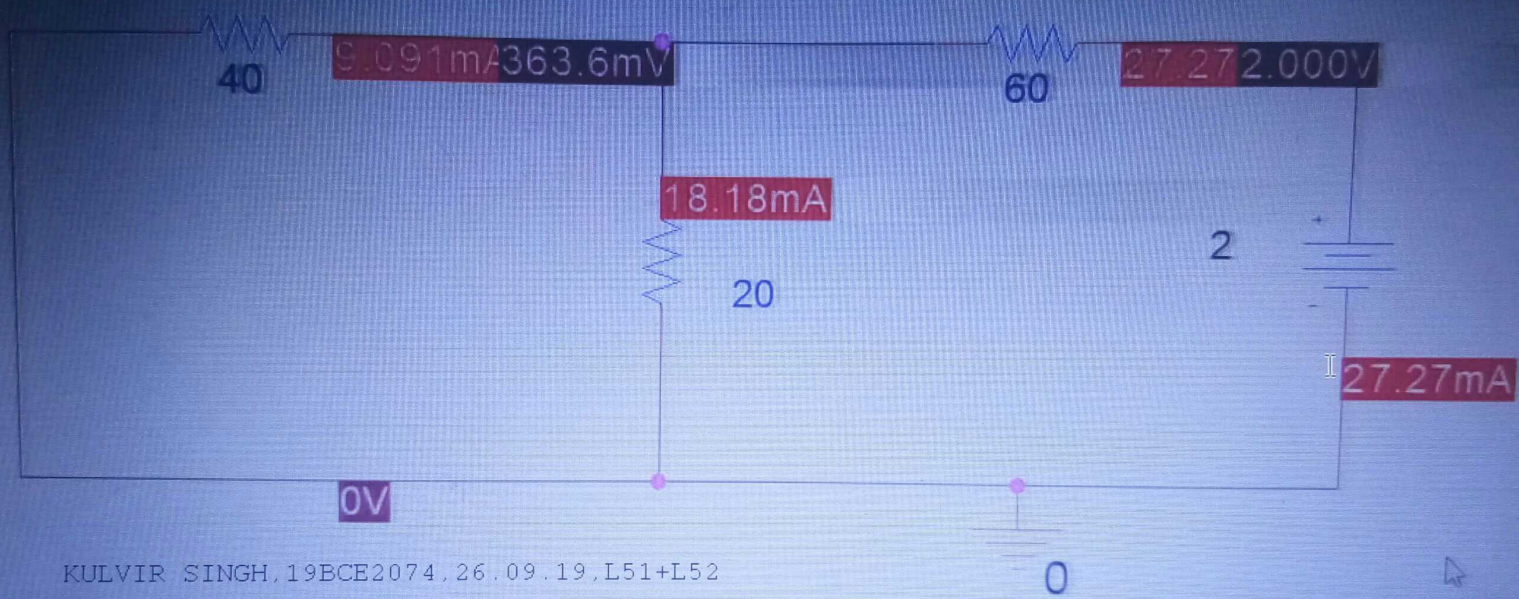

KULVIR SINGH, 19BCE2074, 26.09.19, L51+L52

1 item selected

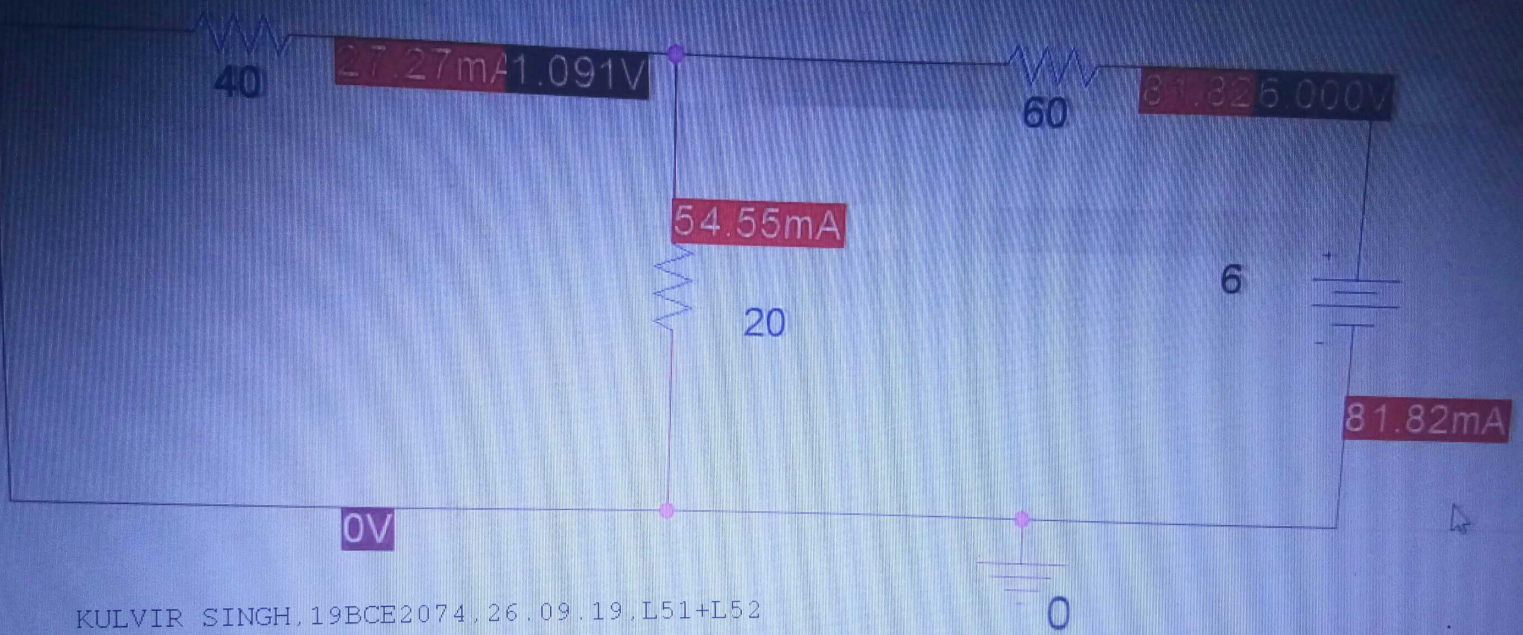

KULVIR SINGH, 19BCE2074, 26.09.19, L51+L52

0 items selected

