

Response of RLC Series Circuit


Aim: To determine and verify the resonant current and resonant frequency for the given series RLC circuit, theoretical and simulation values.

Apparatus/Tool required:

ORCAD / Capture CIS --> Analog Library - R, L & C
Source Library - Vac
Ground (GND) - 0 (zero)

Simulation Settings: Analysis Type - Transient (Time Domain)
Run to time: 20ms

Circuit Diagram:

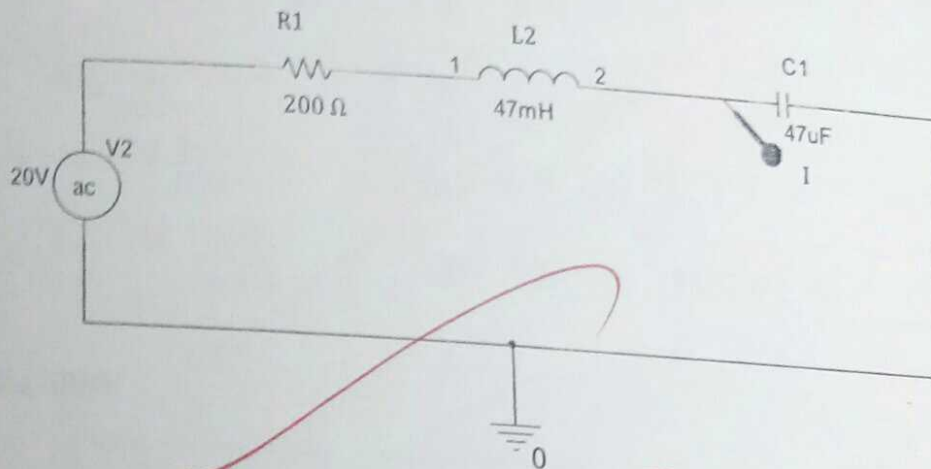


Theory: $Z = R$

$$I = \frac{V}{Z} = \frac{V}{R = (Z_r)}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$I = \frac{V}{Z}$$

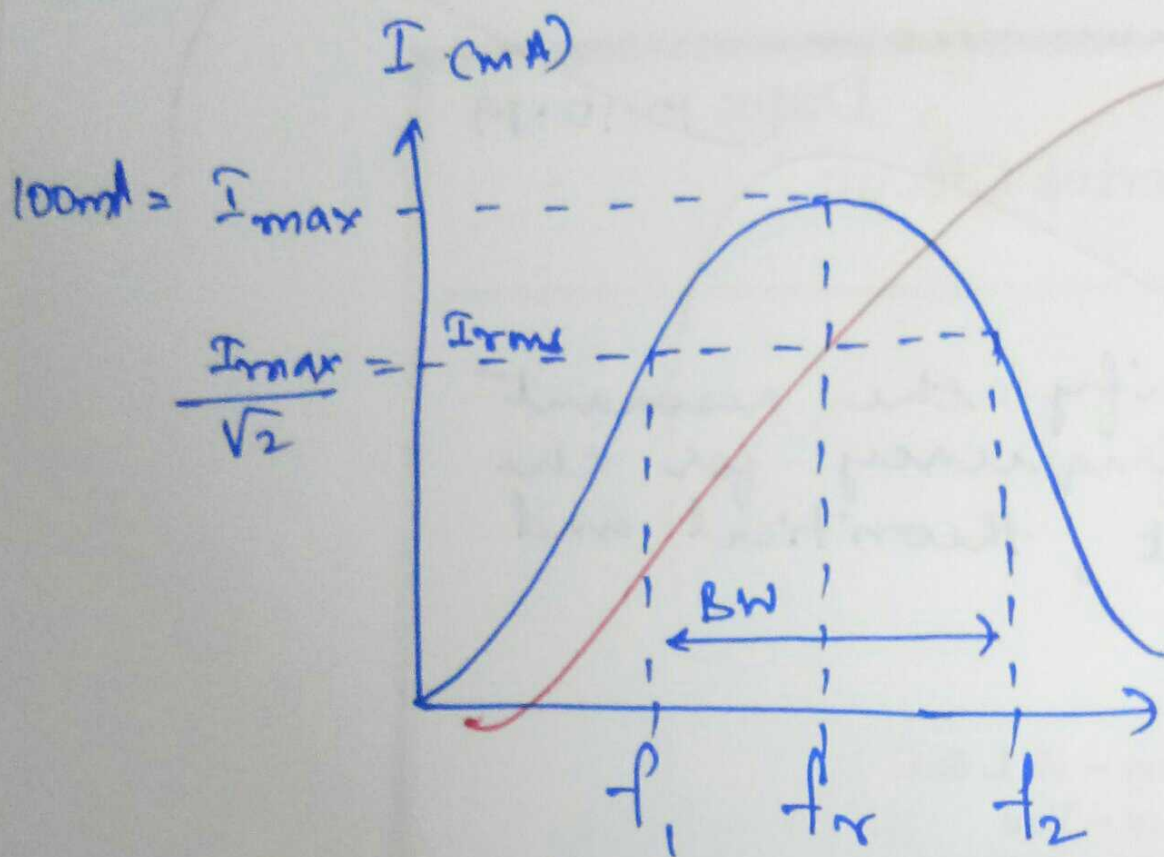

$BW \Rightarrow$ Bandwidth.

Formulae:

$$X_{Lr} = X_{Cr}$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$4\pi^2 f_r^2 LC = 1$$

$$f_r^2 = \frac{1}{4\pi^2 LC}$$

Calculation:

$$f_r = \frac{\sqrt{1}}{\sqrt{4\pi^2 LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$


$$f_r = \frac{1}{2\pi \sqrt{47 \times 10^{-3} \times 47 \times 10^{-6}}}$$

$$f_r = 107.1 \text{ Hz}$$

$$I_r = V/2 = V/2r = R$$

$$I_r = \frac{20}{200} = 0.1 \text{ A} = 100 \text{ mA}$$

Model Graph:

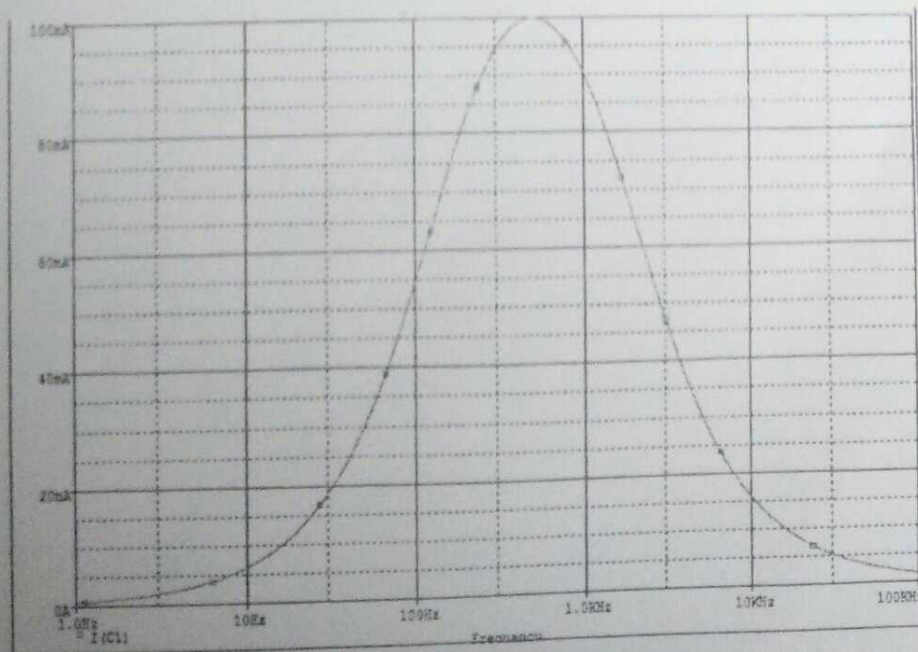

~~10/10/19~~


Result:- The series resonance RLC circuit have been performed in simulation, and the following theoretical and simulation values have been tabulated.

Parameter	Theory value	Simulation values.
I_R	100 mA	100 mA
f_r	107.1 Hz	107.1 Hz

Inference:-

Reg. No: 19 BCE 2014 Name: Kulvir Singh

Date: 10/10/19

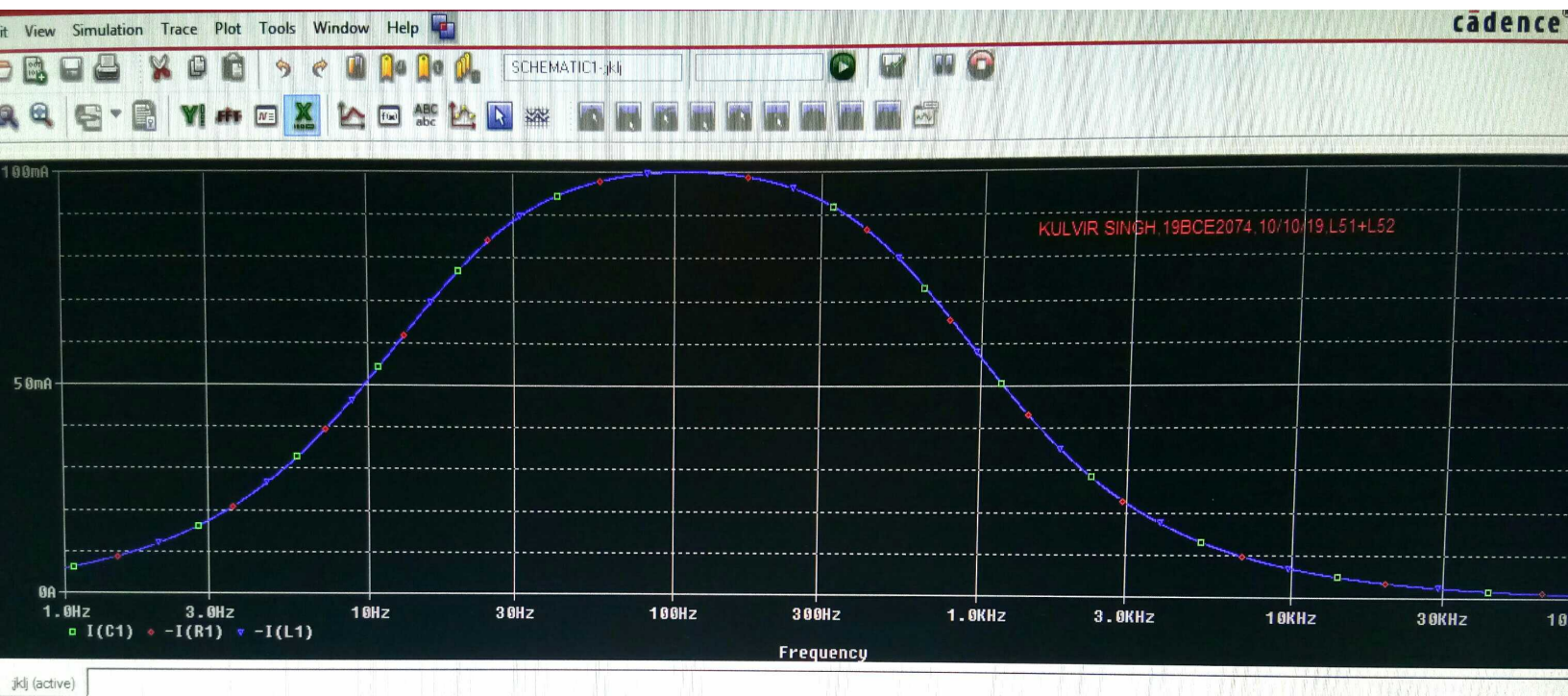

KULVIR SINGH, 19BCE2074, 10/10/19, L51+L52

