

Verification of NETWORK THEOREMS

(Thevenin's Theorem)


Aim: To verify Thevenin's Theorem of given network by theoretical and simulation values

Apparatus/Tool required:

ORCAD / Capture CIS --> Analog Library - R,
Source Library - Vdc, Idc &
Ground (GND) - 0 (zero)


Simulation Settings: Analysis Type - Bias Point

Circuit Diagram

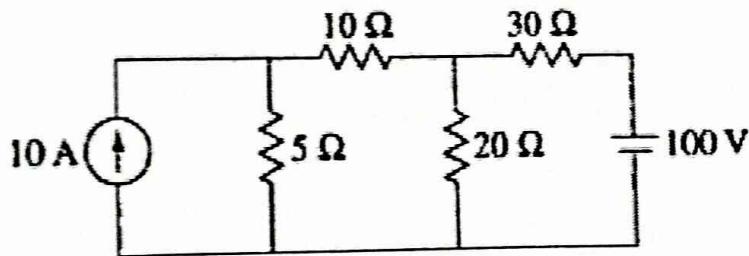


Statement: Thevenin's Theorem

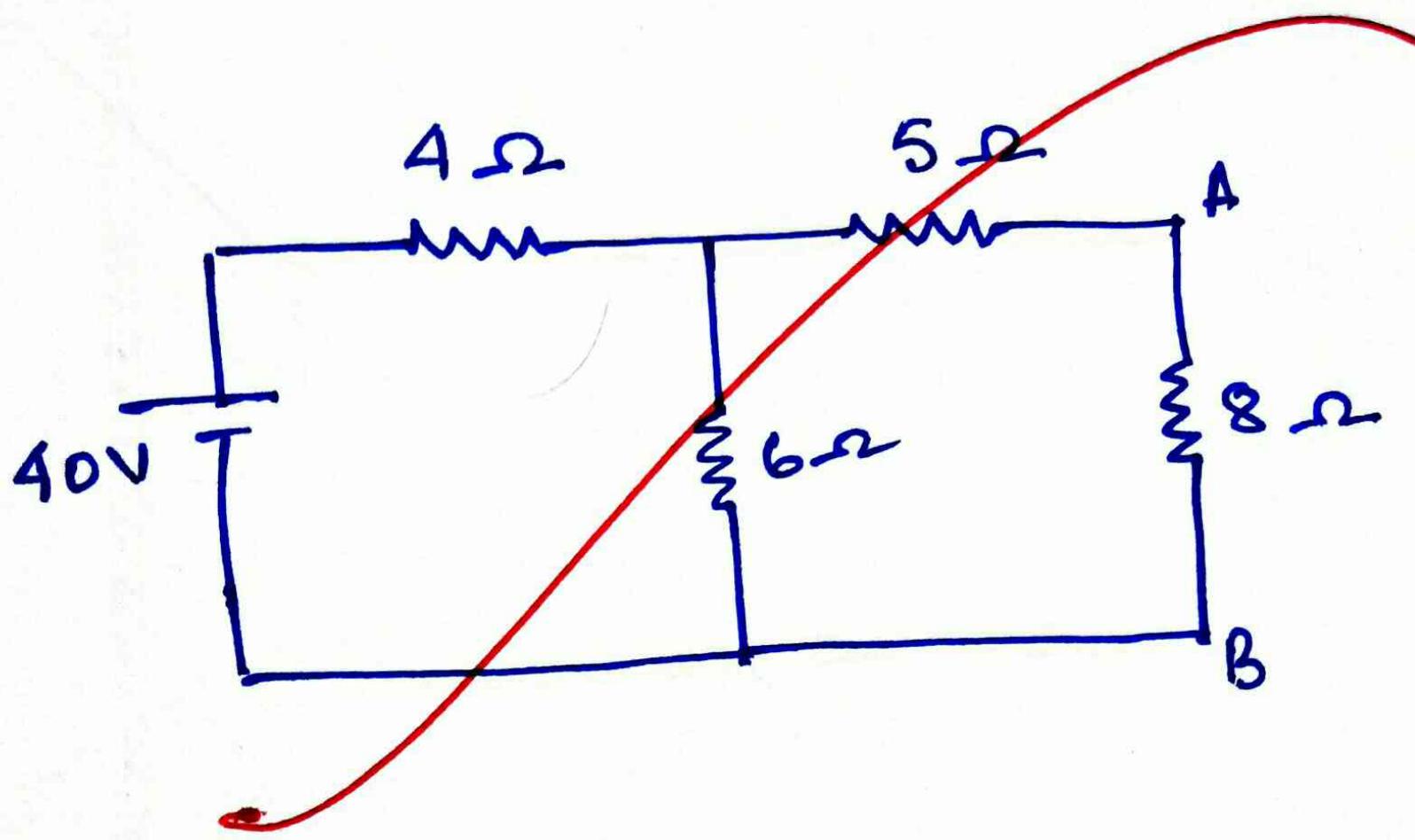In a linear bilateral network with output terminals A and B can be replaced by a single voltage source in series with equivalent resistance.



Manual Calculations:

To Find V_{AB} :

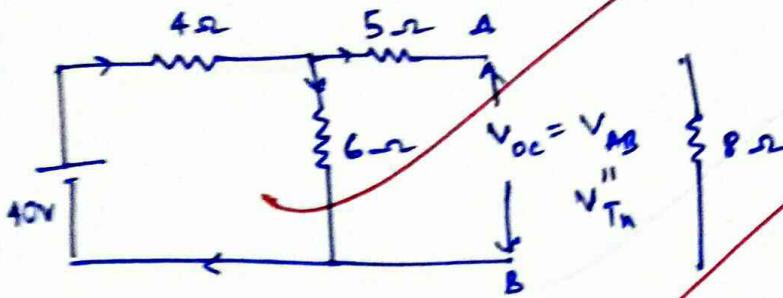


$$I = \frac{V}{R_T} = \frac{40}{4+6} = 4A$$

$$V_{Tn} = V_{AB} = V_{DC} = IR = 4 \times 6 = 24V$$

~~• 6000 bcdel 6000~~
~~• 6000 / 6000 = 1000~~


To Find R_{AB} :

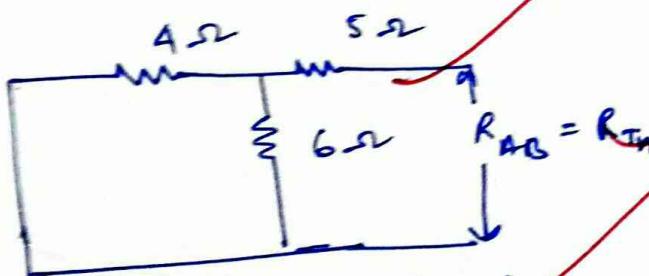

$$\begin{aligned} R_{Tn} &= R_{AB} = (4||6) + 5 \\ &= \left(\frac{4 \times 6}{4+6} \right) + 5 \\ &= \frac{24}{10} + 5 \\ &= 2 \cdot 4 + 5 = 7\Omega \end{aligned}$$

To Find I_L :

Equivalent Circuit

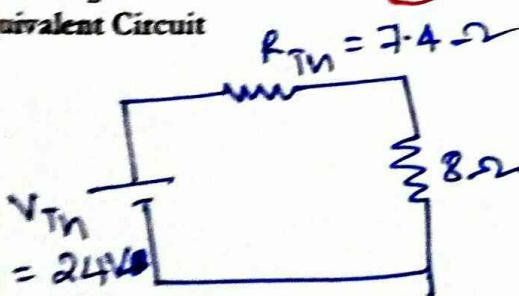


$$I_L = \frac{V_{Tn}}{(R_{Tn} + R_L)}$$

$$= \frac{24}{7.4 + 8}$$


$$= \frac{24}{15.4} = 1.55A$$

Simulation Circuit:

To Find V_{ab} :

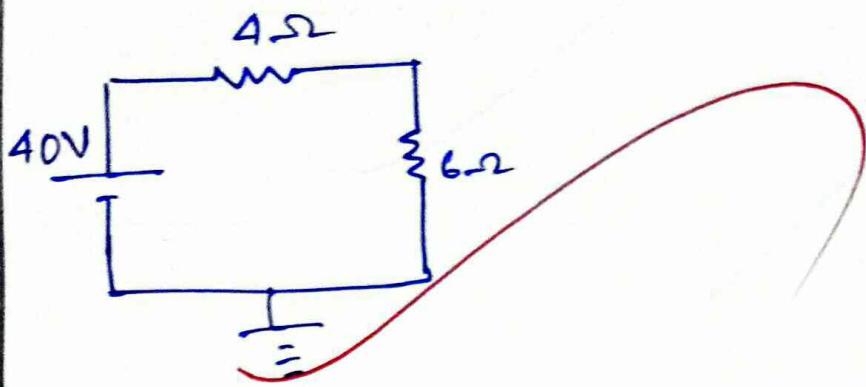


To Find R_{th} :

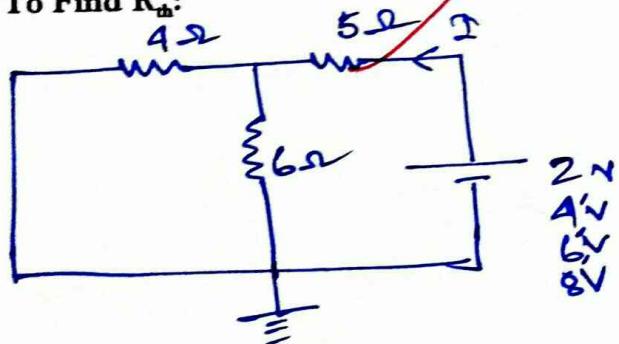

$V(V)$	$I(A)$	$R = V/I$
2	0.703	2.85 Ω
4	0.505	7.9 Ω
6	0.408	14.6 Ω

$$R_{avg} = 7.40 \Omega$$

To Find I_L :

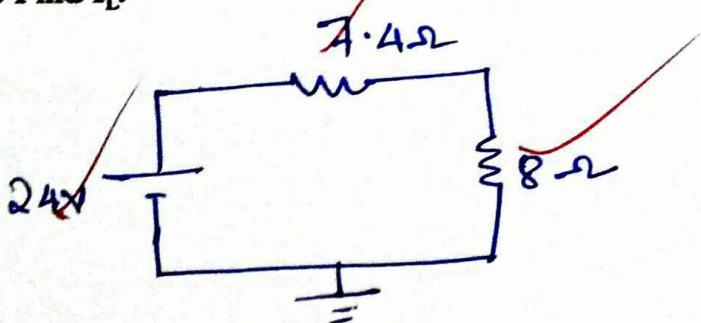

Result:


Manual Calculations

Thevenin's Theorem


	Theoretical Values	Simulated Result
V_{Th}	24 V	24 V
R_{Th}	7.4 Ω	7.4 Ω
I_L	1.55 A	1.55 A

Inference: The Thevenin's Theorem has been verified by theoretical values and simulation values.

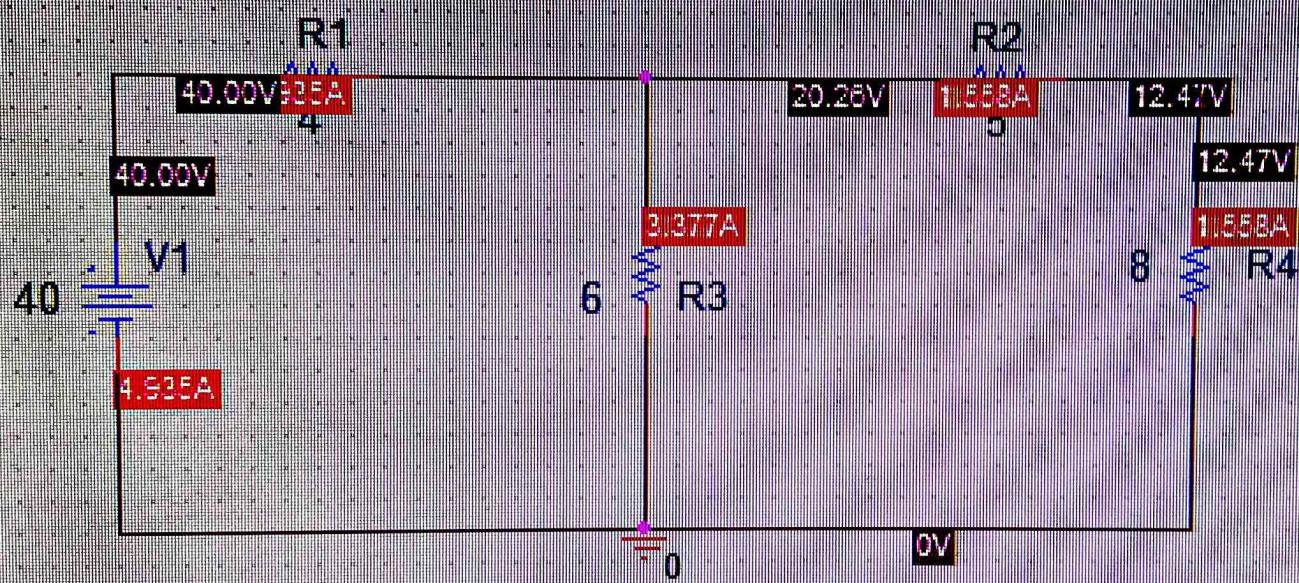
Reg. No: 19BCE2074 Name: KULVIR SINGH Date: 19.9.19




19BCE2074 , KULVIR SINGH , 19.09.2019

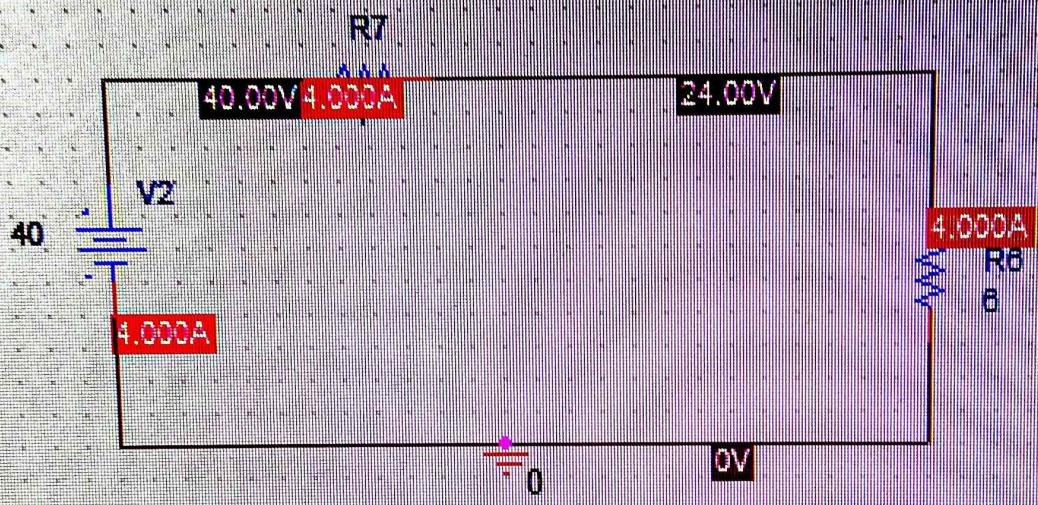


19BCE2074 , KULVIR SINGH , 19.09.2019

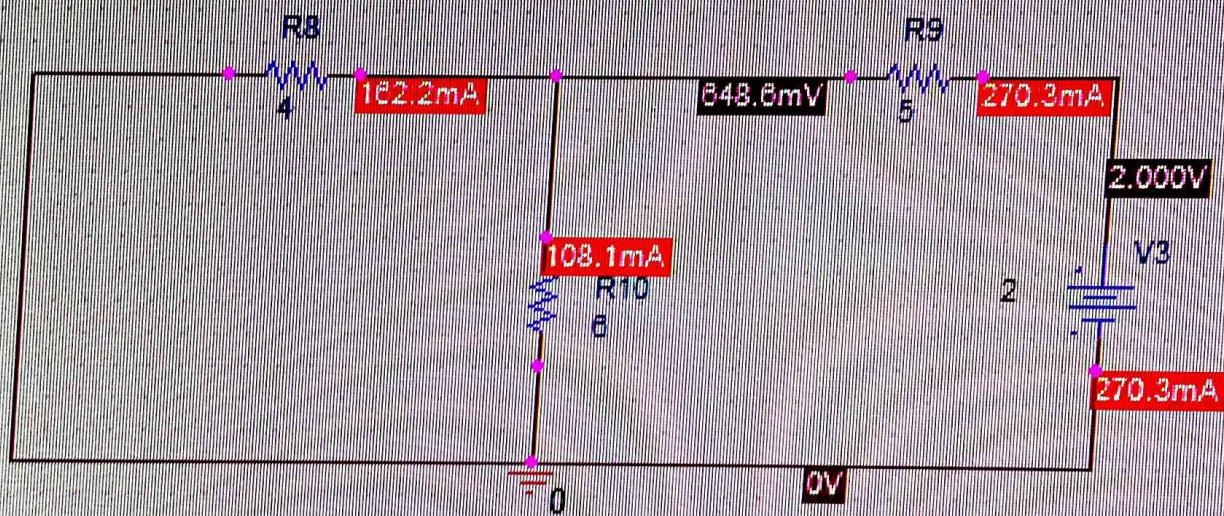


19BCE2074 , KULVIR SINGH , 19.09.2019

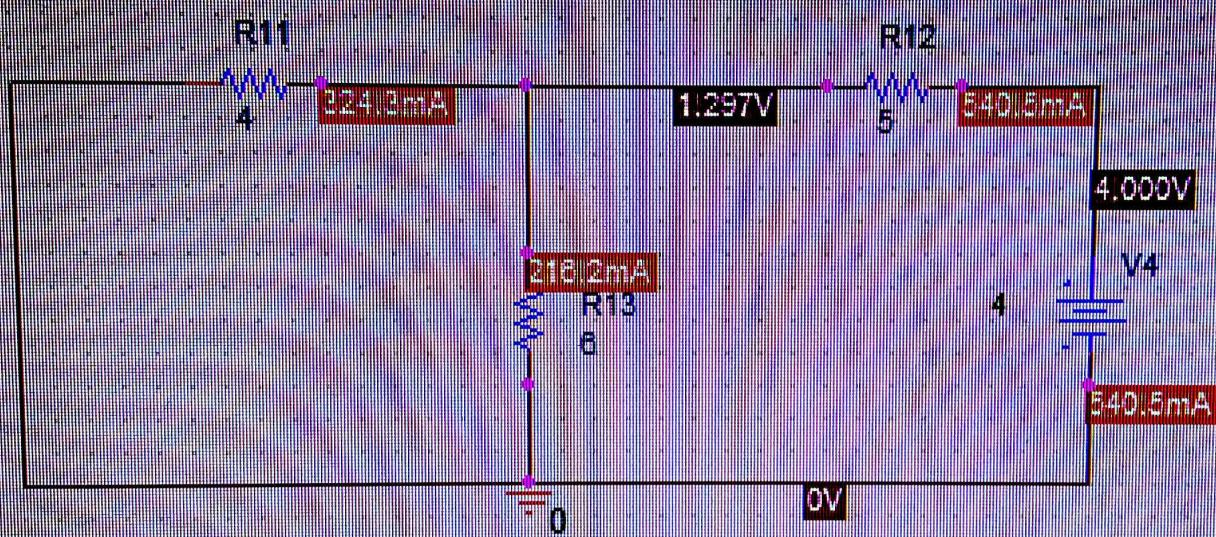

19BCE2074 , KULVIR SINGH , 19.09.2019

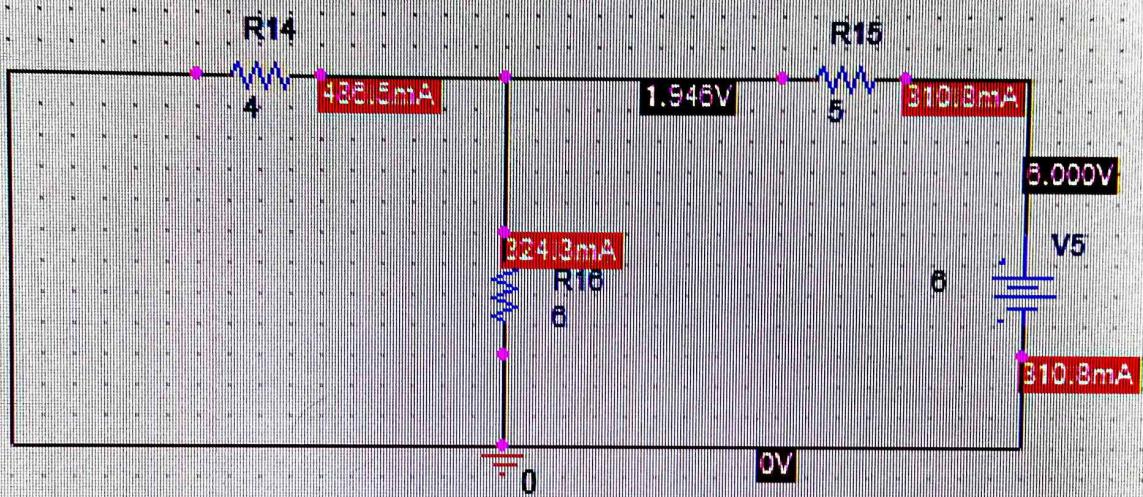

19BCE2074 , KULVIR SINGH , 19.09.2019

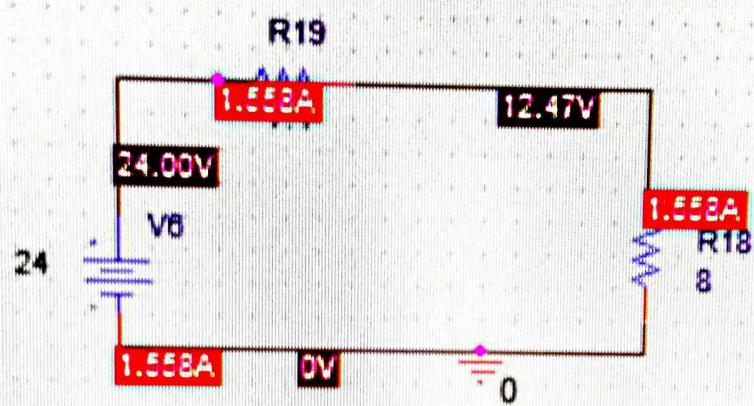

19BCE2074 , KULVIR SINGH , 19.09.2019