

Ex. No.:4

Design of Half Adder Circuit using gates


Date: 28.08.19

Aim: To verify the truth tables for half adder circuit using logic gates

Apparatus Required:


S. No.	Name of the apparatus	Range / Type	Quantity
1	7486 gate	-	1 No.
2	7408 gate	-	1 No.
3	LED	-	1 No.
4	RPS	-	2 Nos.
5	Resistor	0 - 15 V	1 No.
6	Breadboard	330 Ω	2 Nos.
7	Wires	-	1 No.
		-	Few

Circuit Diagram:

 


Theory: Logic Gates


OR-gate

 


A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

 


AND - gate

 


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

 


XOR - gate

 

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

 

NOT - gate

 

$$\bar{1} = 0$$

$$\bar{0} = 1$$

Truth Table

A	B	$S=A \oplus B$	$C=A.B$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Observation:

Procedure:

Result: The design of half adder circuit has been verified with truth tables

Reg. No: 19BCE2074 Name: Kulvir Singh

Date: 29.8.19