
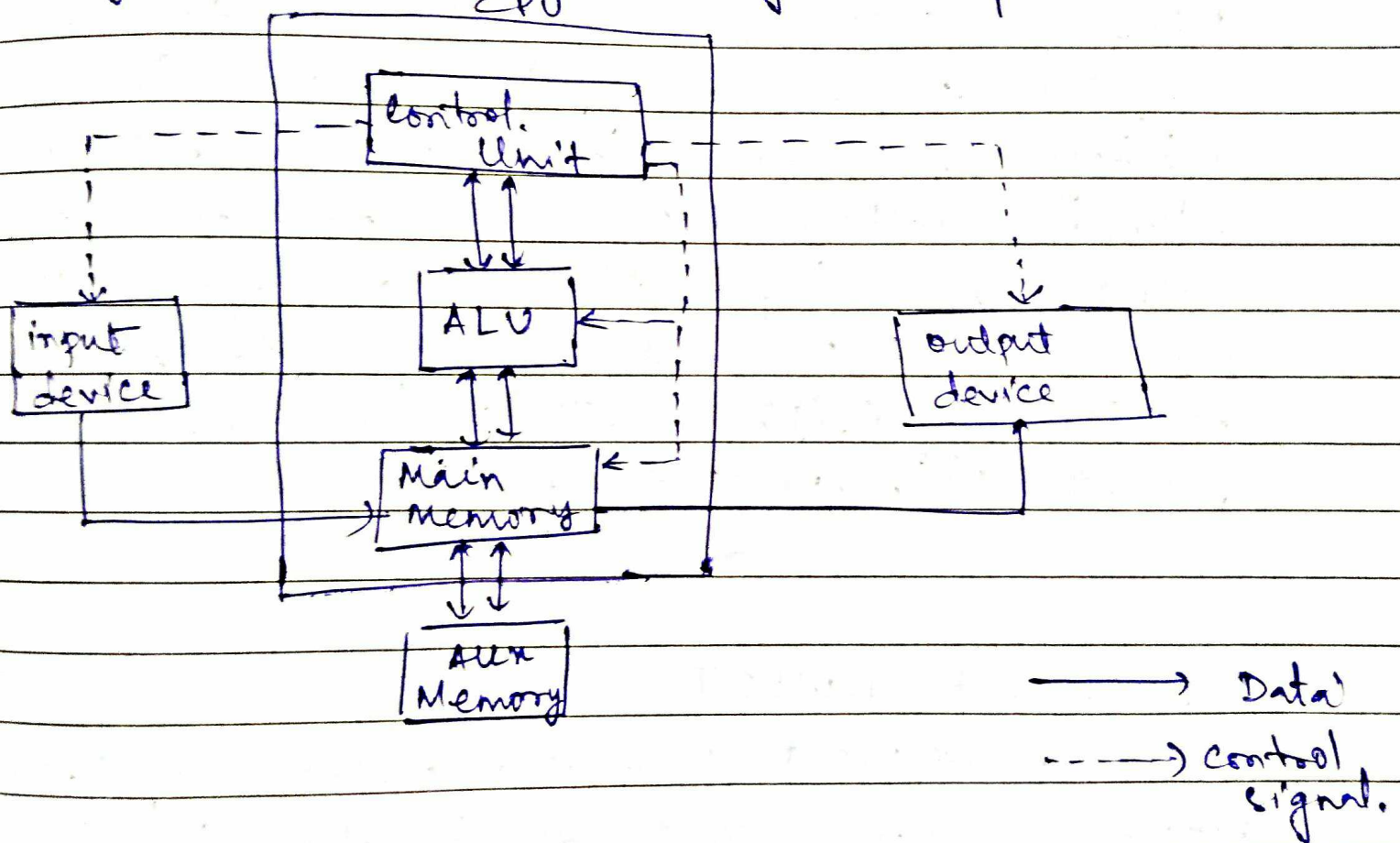


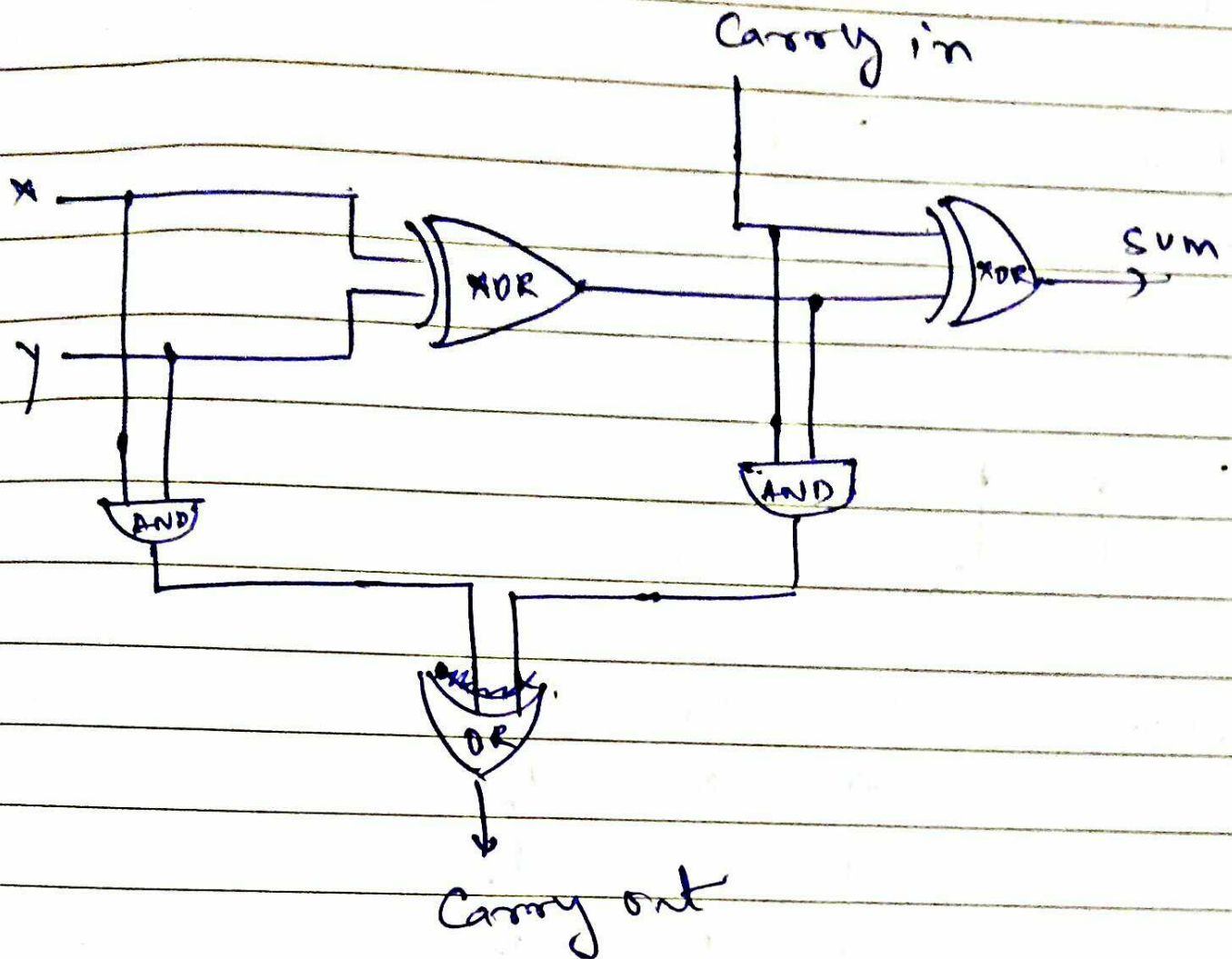1) Organisation of Basic Digital Computer



2) Full Adder




INPUT

OUTPUT

| X | Y | Carry in | Sum | Carry out |
|-----|-----|----------|-----|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

3)


4:1 Mux

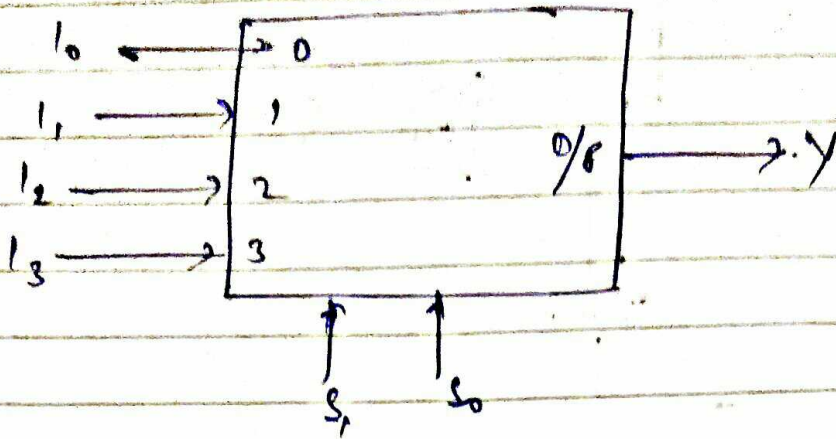

Truth Table


| S_1 | S_0 | Y |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

Logic Diagram

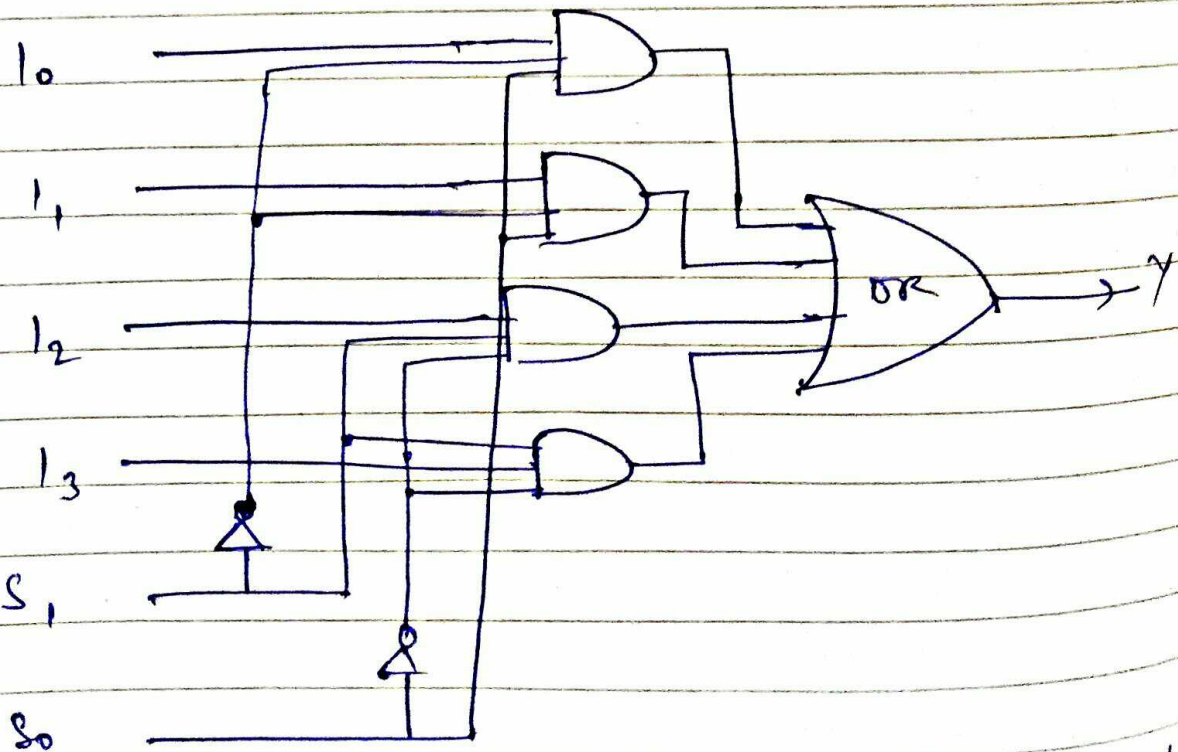


$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$


1 in 4 demux

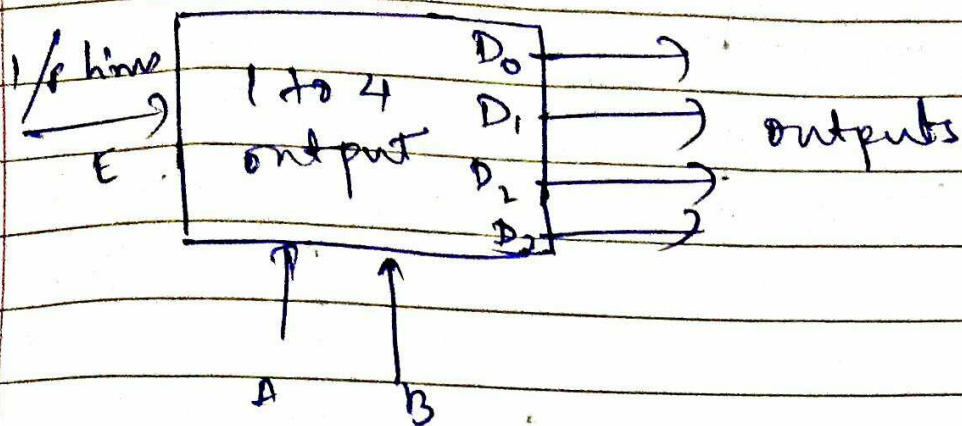

| E 1/p | Select | | O/p | | | |
|----------|--------|---|----------------|----------------|----------------|----------------|
| | A | B | D ₀ | D ₁ | D ₂ | D ₃ |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

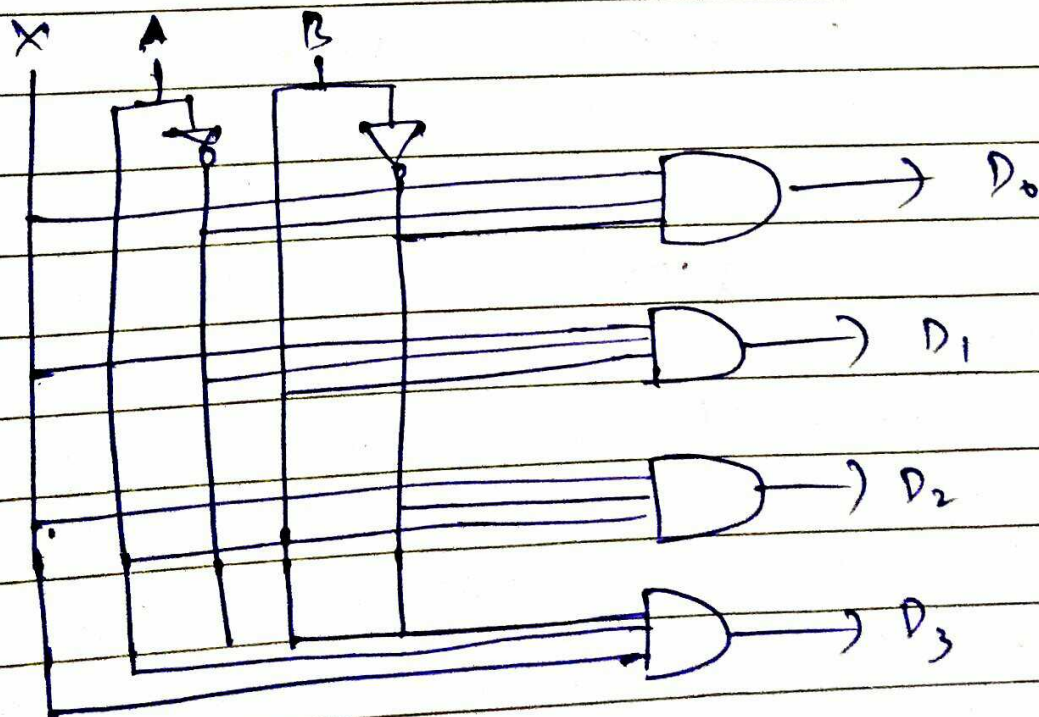



A) IV Characteristics:

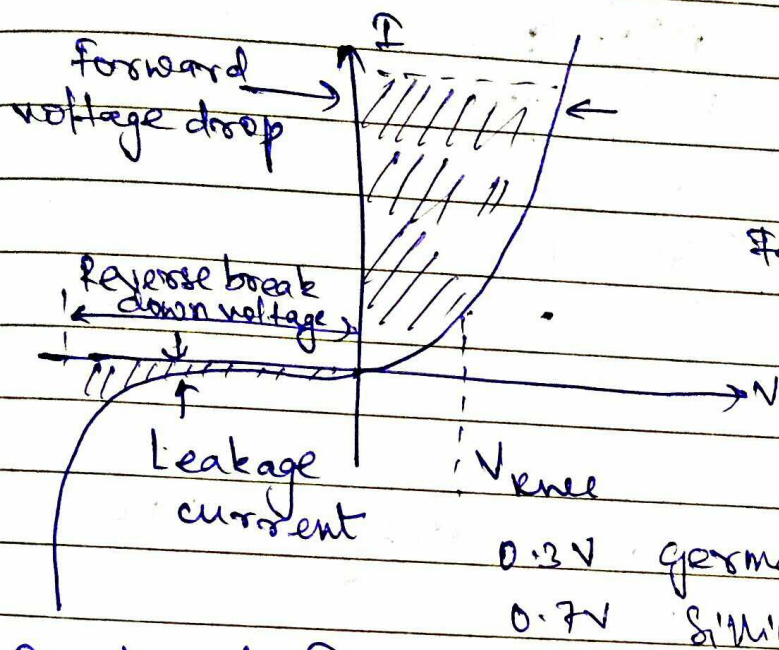

Quadrant I
Forward Operating Region

Quadrant II
Reverse operating region



Conventional Current Flow

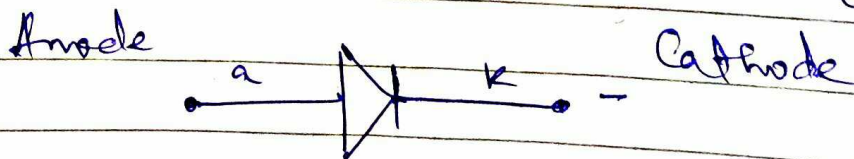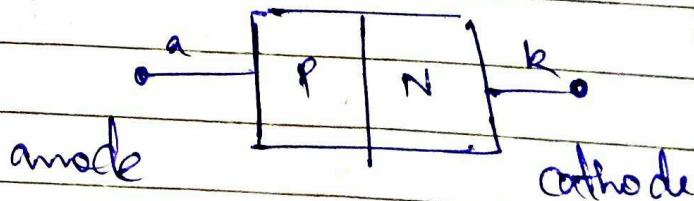

5) Forward Biased PN Junction Diode

When a diode is connected in a Forward Bias condition, a negative voltage is applied to the N-type material a positive voltage to the P-type material. If this external voltage becomes greater than the value of the potential barrier, approx 0.7 volts for Si and 0.3 volts for Ge, the potential barrier opposition will be overcome and current will start to flow.


7)

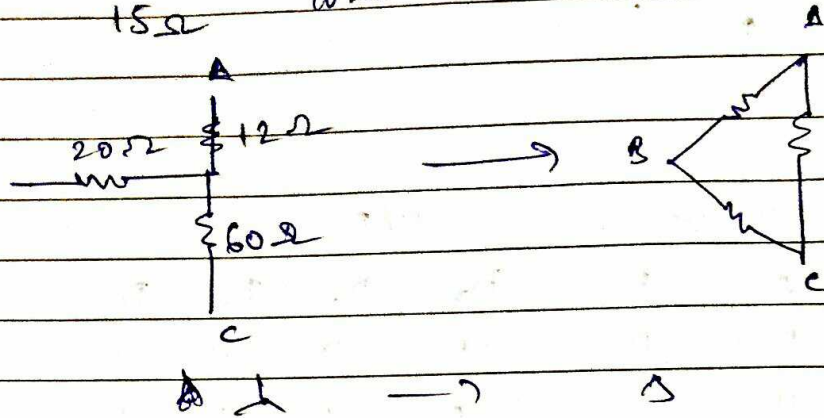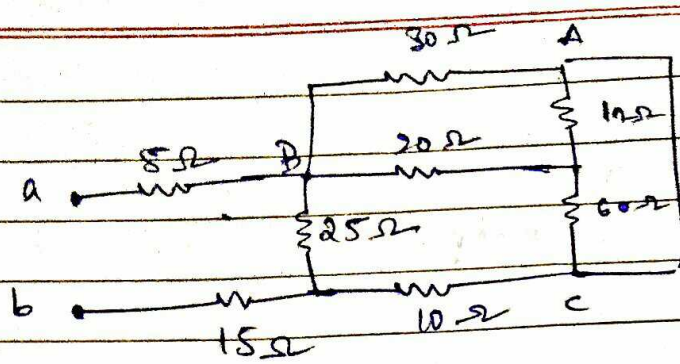

$$R_{AB} = 12 + 20 + \frac{12 \times 20}{60} = 36 \Omega$$


$$R_{BC} = 80 + 60 + \frac{12 \times 60}{12} = 180 \Omega$$
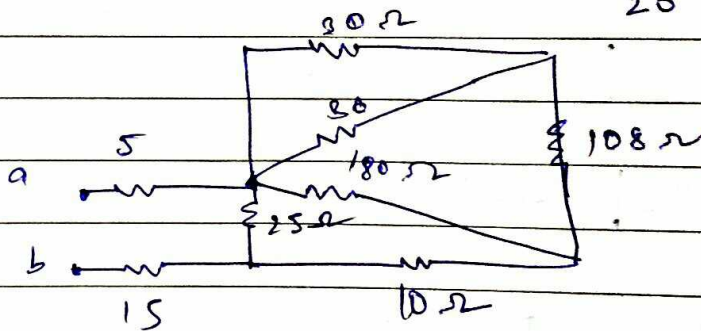
$$R_{AC} = 12 + 60 + \frac{12 \times 30}{20} = 108 \Omega$$



$$30 \parallel 36 = \frac{30 \times 36}{66} = 20 \Omega$$
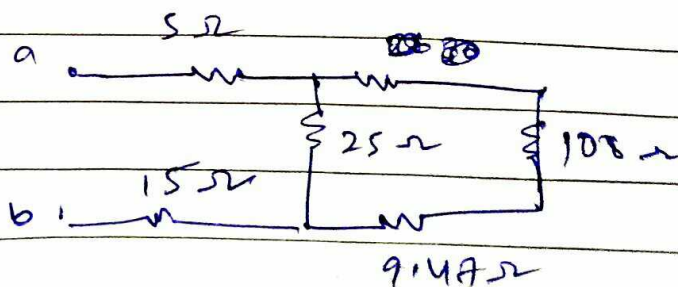
$$180 \parallel 10 = \frac{1800}{190} = 9.47 \Omega$$




$$R_{eq} = \left\{ (26 + \cancel{9.41}) \parallel 25 \right\} + 5 + 15$$

$$= \left(\frac{35.5 \times 25}{60.5} \right) + 14.62 \Omega + 5 + 15$$

$$= \underline{\underline{36.67 \Omega}} \quad \leftarrow \text{Ans}$$

9) $f = 60 \text{ Hz}$

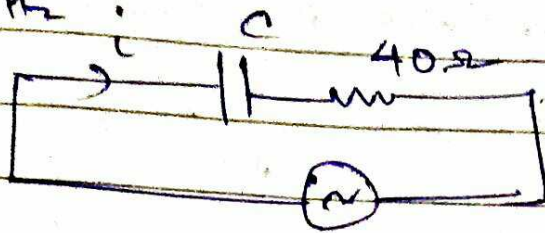

$I = 3 \text{ A}$

$Z = 50 \Omega$

a) $Z = \sqrt{R^2 + X_C^2}$

$\Rightarrow 50^2 - 40^2 = \left(\frac{1}{2\pi fC}\right)^2$

$\Rightarrow 900 \times 2^2 \times \pi^2 \times 60^2 = \frac{1}{C^2}$

$\Rightarrow C = 8.84 \times 10^{-6} \text{ F}$

$\Rightarrow C = 8.84 \mu\text{F}$


b) $V = IZ$

$\Rightarrow V = 3 \times 50$
 $= 150 \text{ V}$

$\tan \theta = \frac{X_C}{R}$

$= \frac{1}{(2\pi f)R} = \frac{30}{40}$

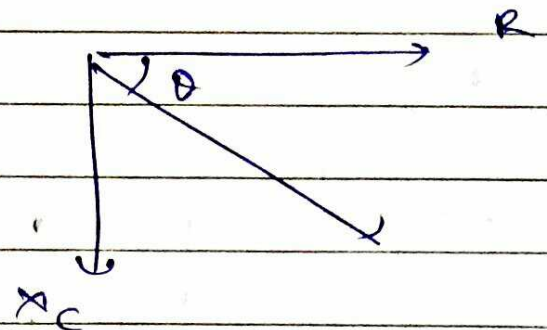$\theta = \tan^{-1} \frac{3}{4} = 36.8^\circ$




d) $V_R = IR = 3 \times 40 = 120 \text{ V}$


$V_C = I X_C = 3 \times \frac{1}{2\pi fC} = 90 \text{ V}$

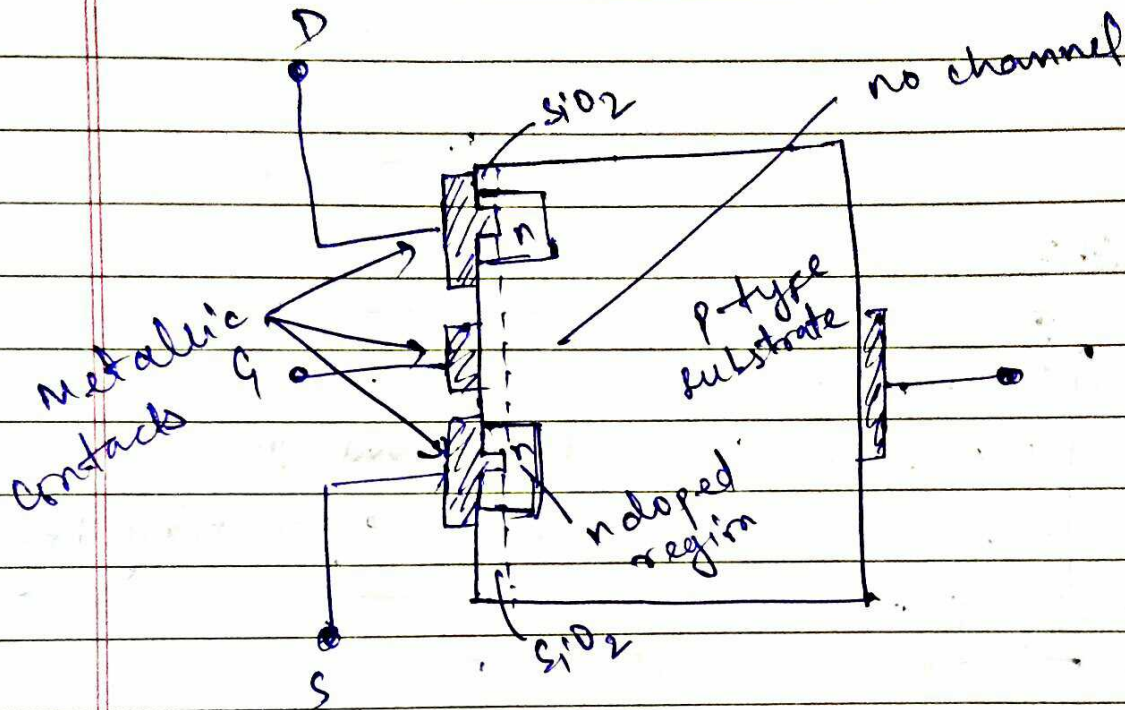10) Enhancement MOSFET



The enhancement has the absence of channel between source and drain terminals.



N-channel enhancement-type MOSFET

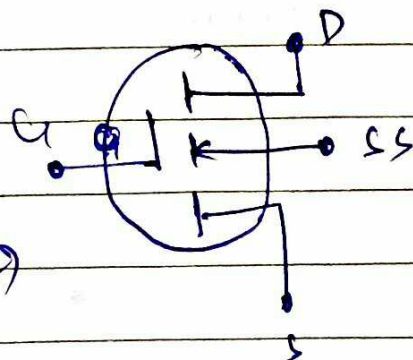

schematic symbol →

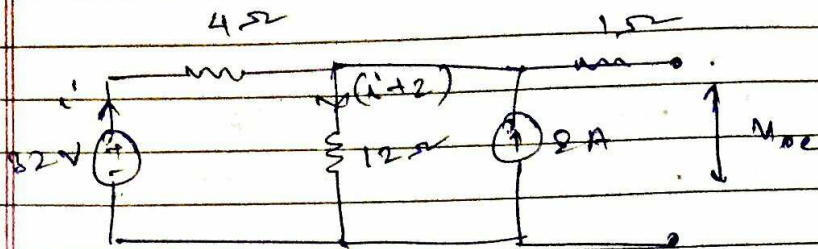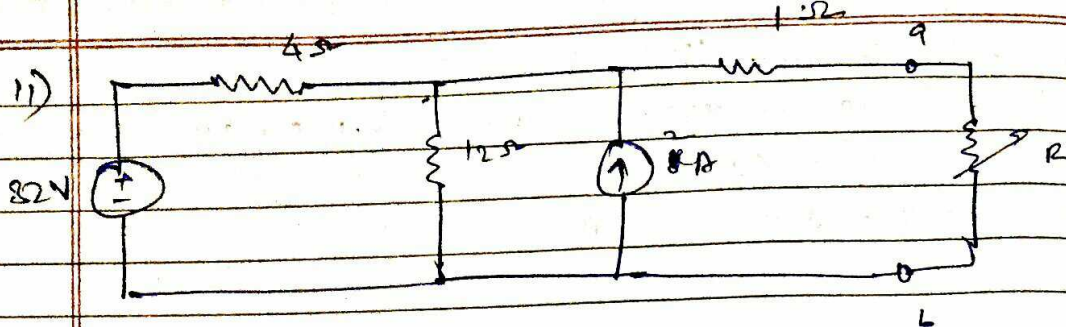

$$+82 - 4i - 12(i+2) = 0$$

$$\Rightarrow 82 = 16i + 24$$


$$\Rightarrow i' = \frac{8}{16}$$

$$\Rightarrow i' = 0.5 \text{ A}$$

$$V_{oc} = (i' + 2) \cdot 12$$


$$= \frac{8}{2} \times 12 = 30 \text{ V}$$

for R_{th}

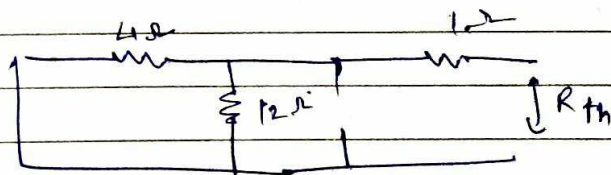

$$12 \parallel 4 + 1$$
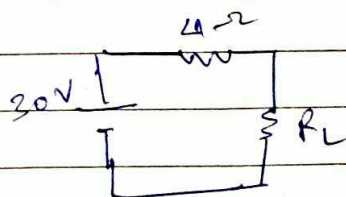
$$R_{th} = \frac{12 \times 4}{16} + 1 = 4 \Omega$$



$$i = \frac{30}{4 + R_L}$$

$$R_L = 6$$

$$i = \frac{30}{4 + 6} = 3 \text{ A}$$

$$R_L = 16$$

$$i = \frac{30}{4 + 16} = 1.5 \text{ A}$$

$$R_L = 36$$

$$i = \frac{30}{4 + 36} = \frac{8}{4} = 0.75 \text{ A}$$