

Experiment No. - 3.


Date : 30-01-2020

Aim:


Design a half adder, full adder, half subtractor, full subtractor using NAND and NOR gates.


Half adder:

using NAND

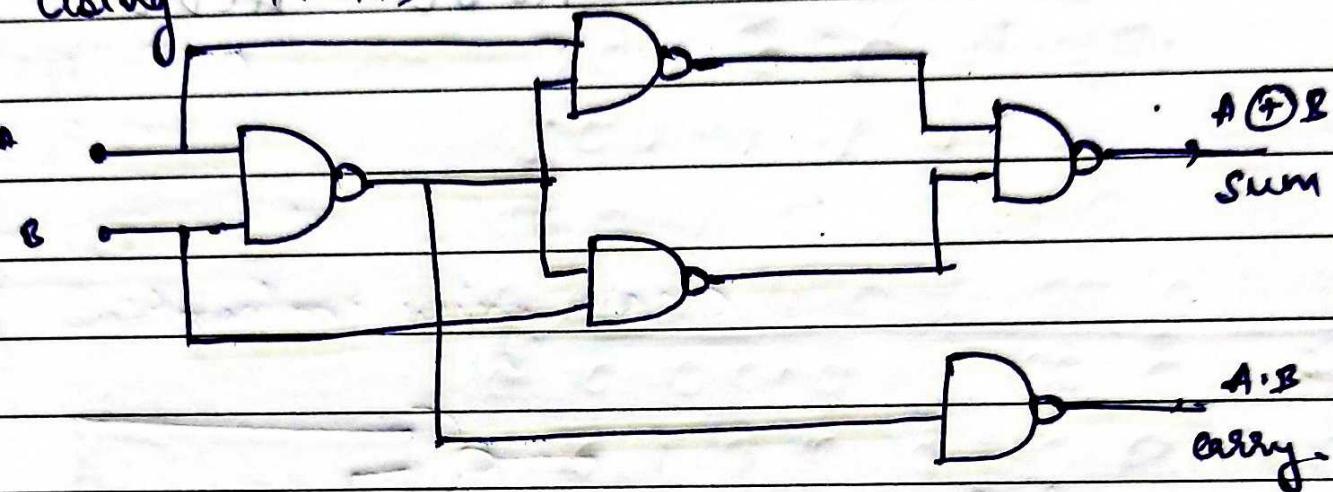

using NOR

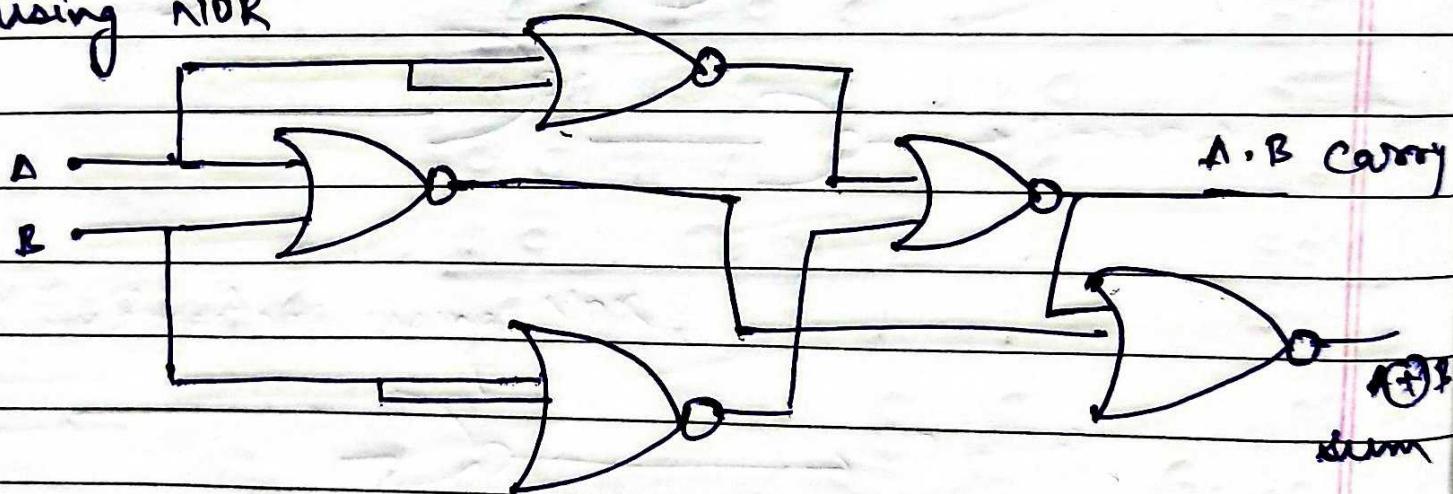


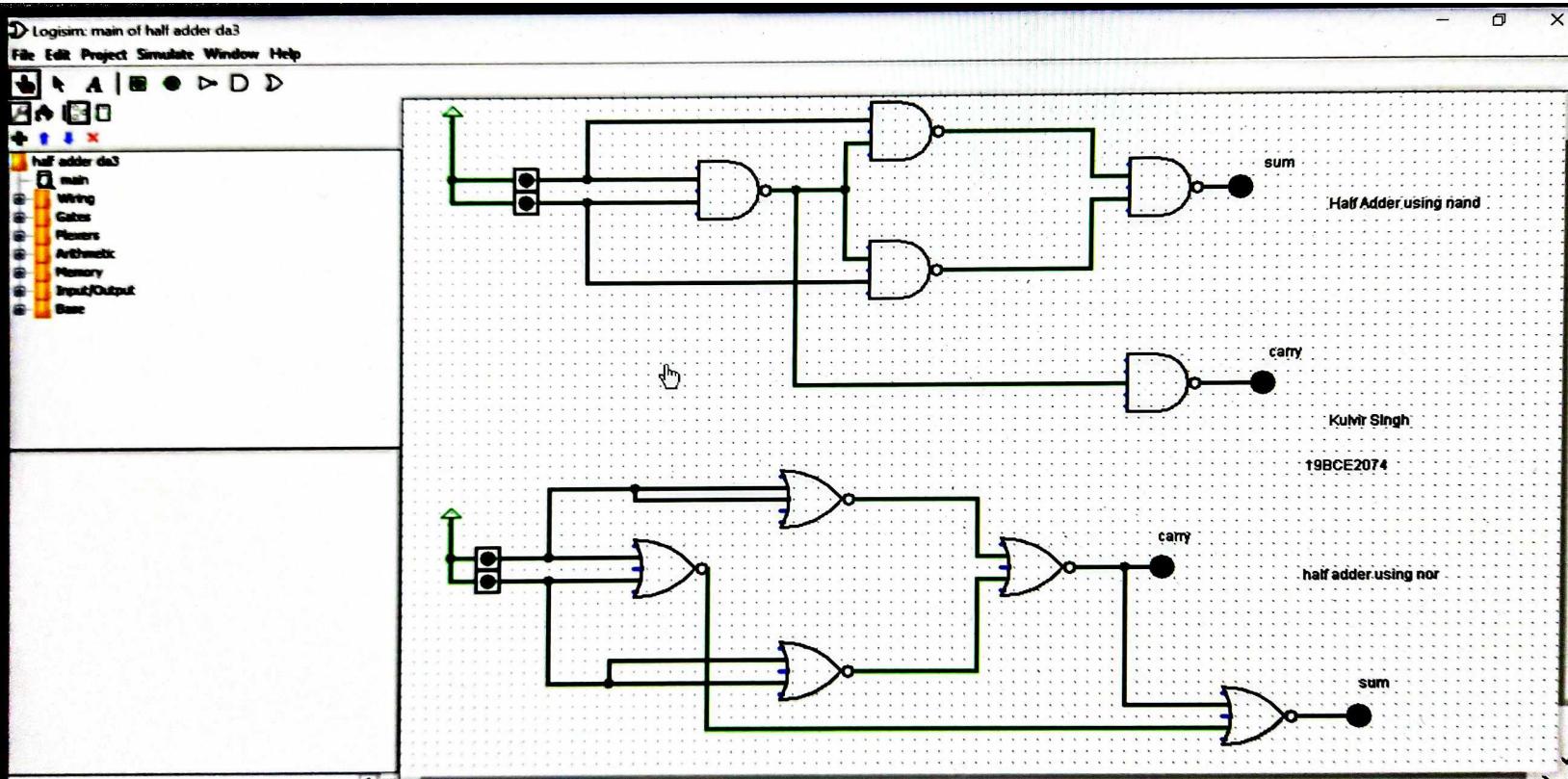


Truth Table


| A | B | Sum A ⊕ B | Carry A · B |
|---|---|--------------|----------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |


Full adder using NAND

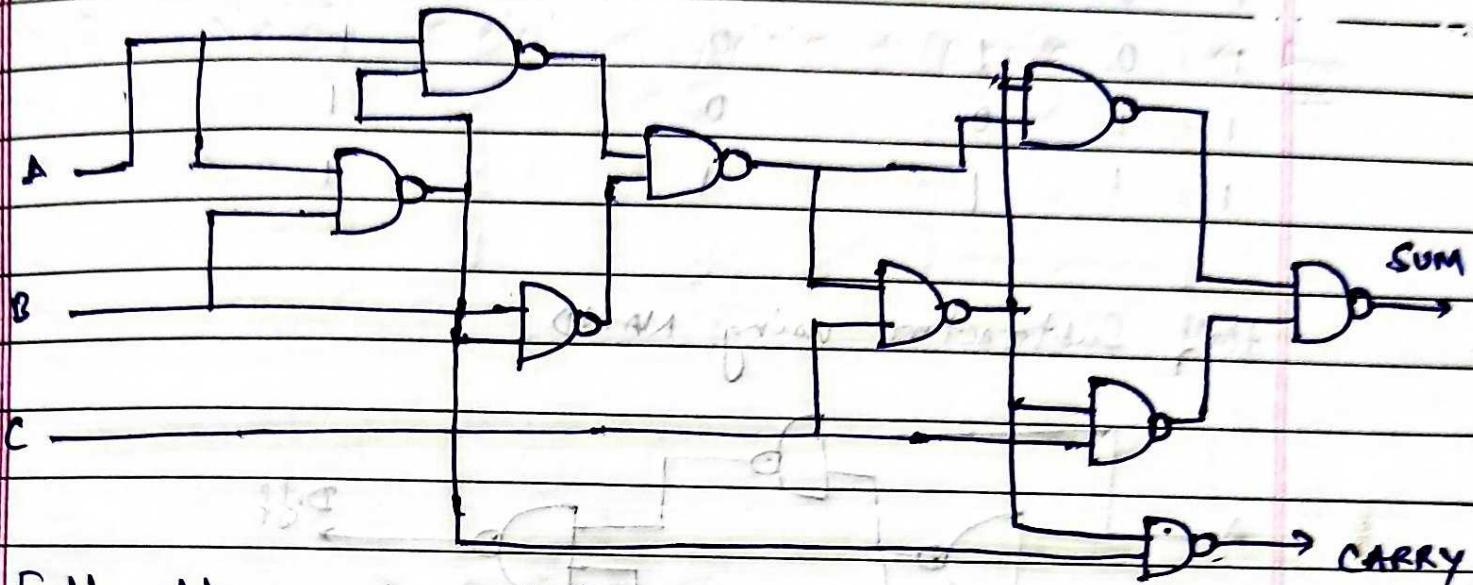

Full adder using NOR

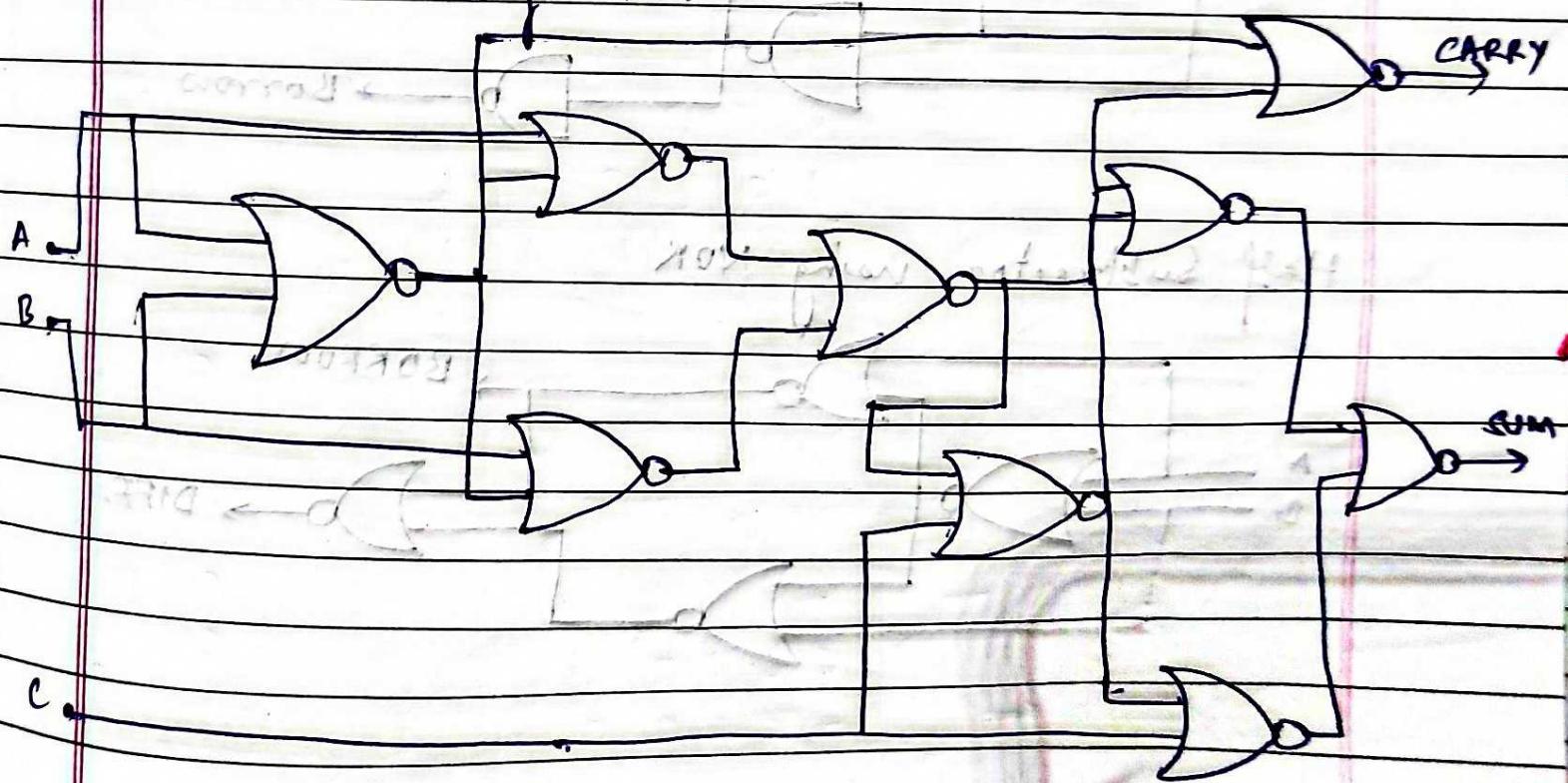

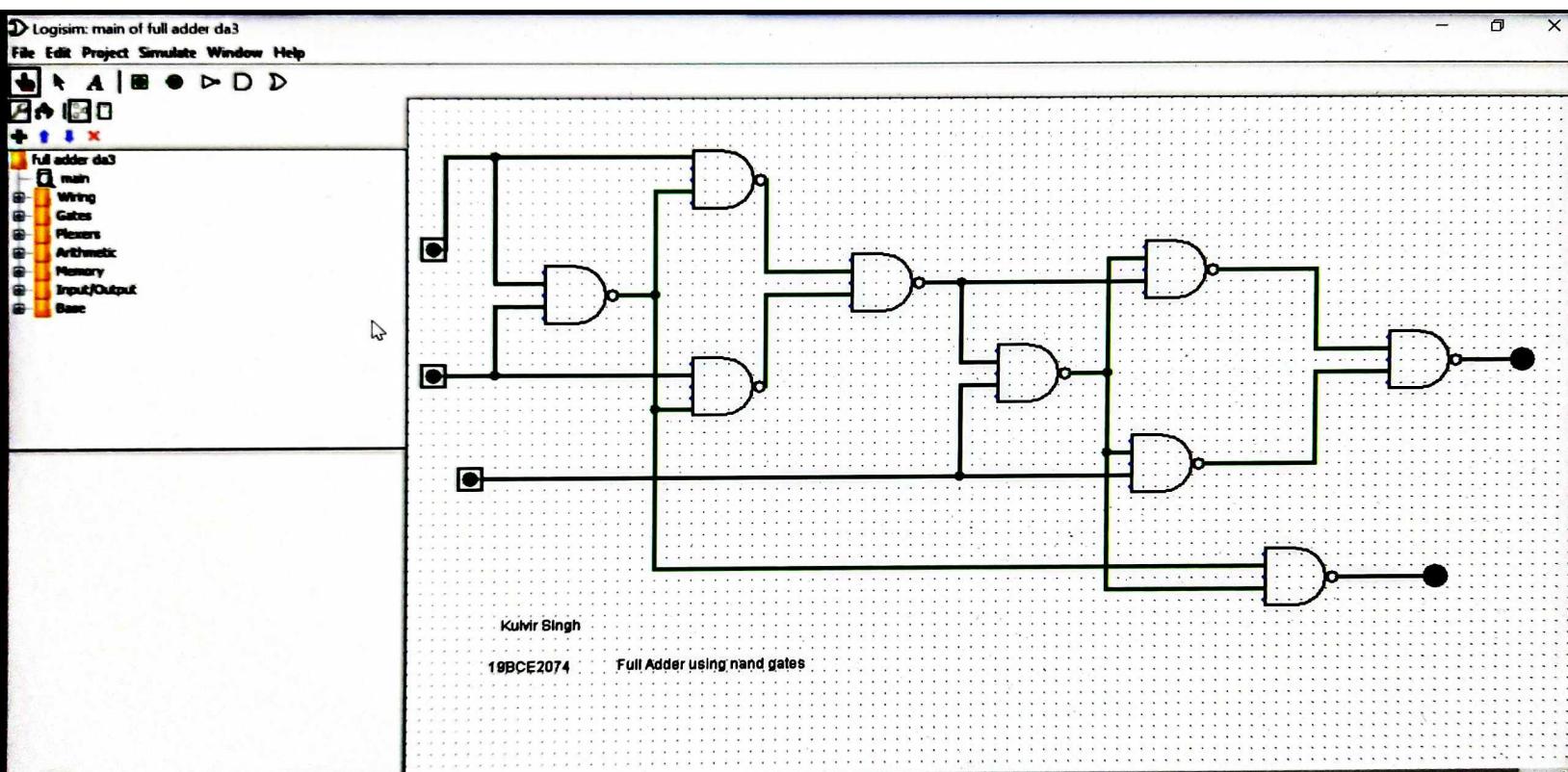


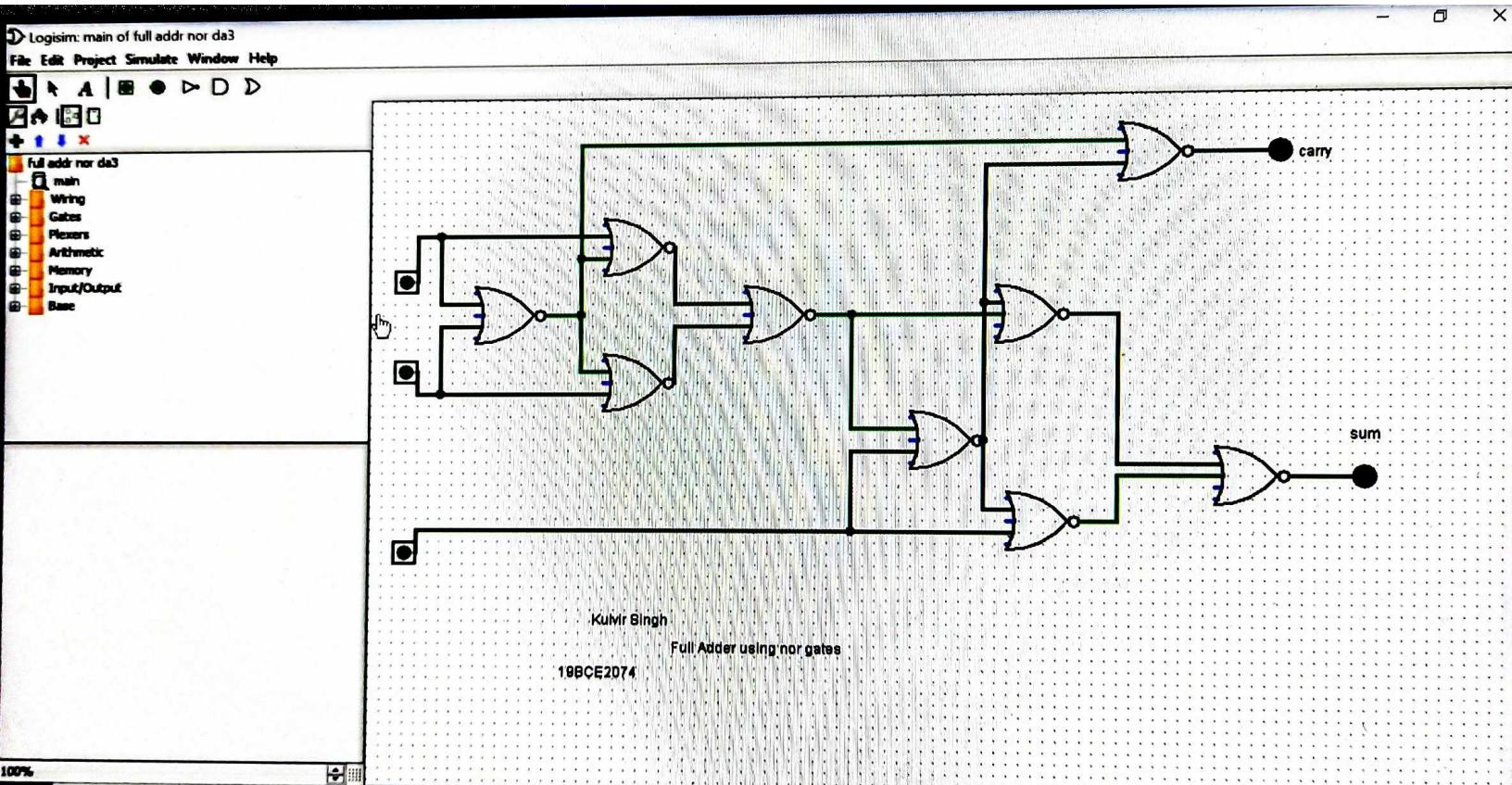


Truth Table


| A | B | C | $A \oplus B \oplus C$ | Carry | Diff |
|---|---|---|-----------------------|-------|------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 |


Half Subtractor using NAND

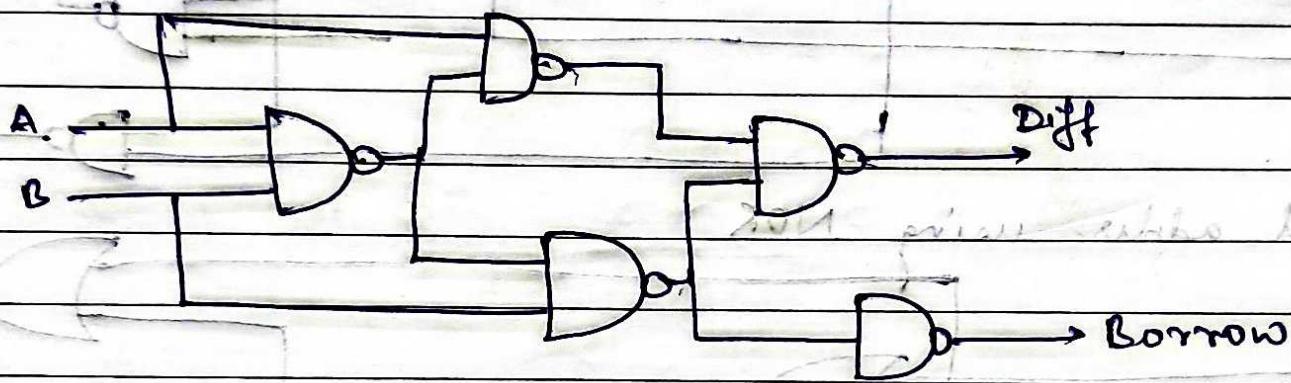

Half Subtractor using NOR

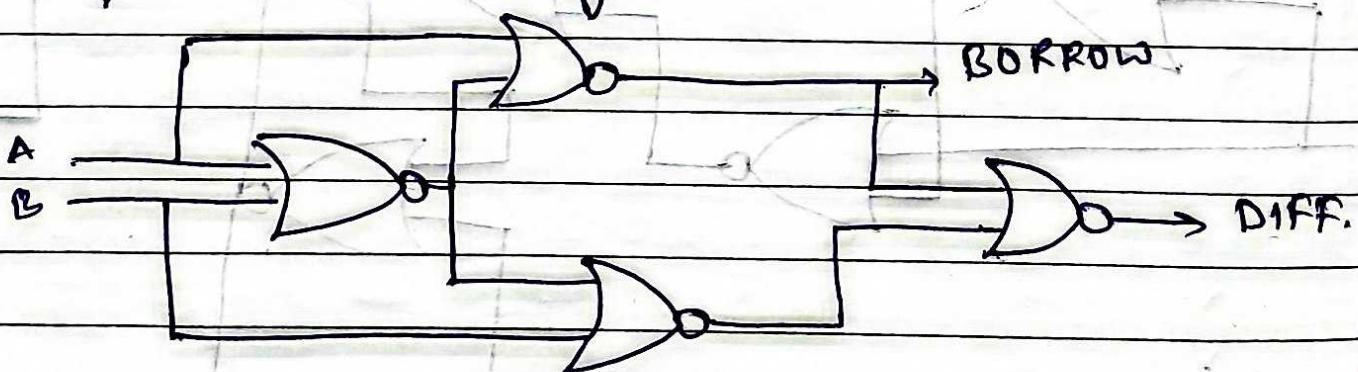

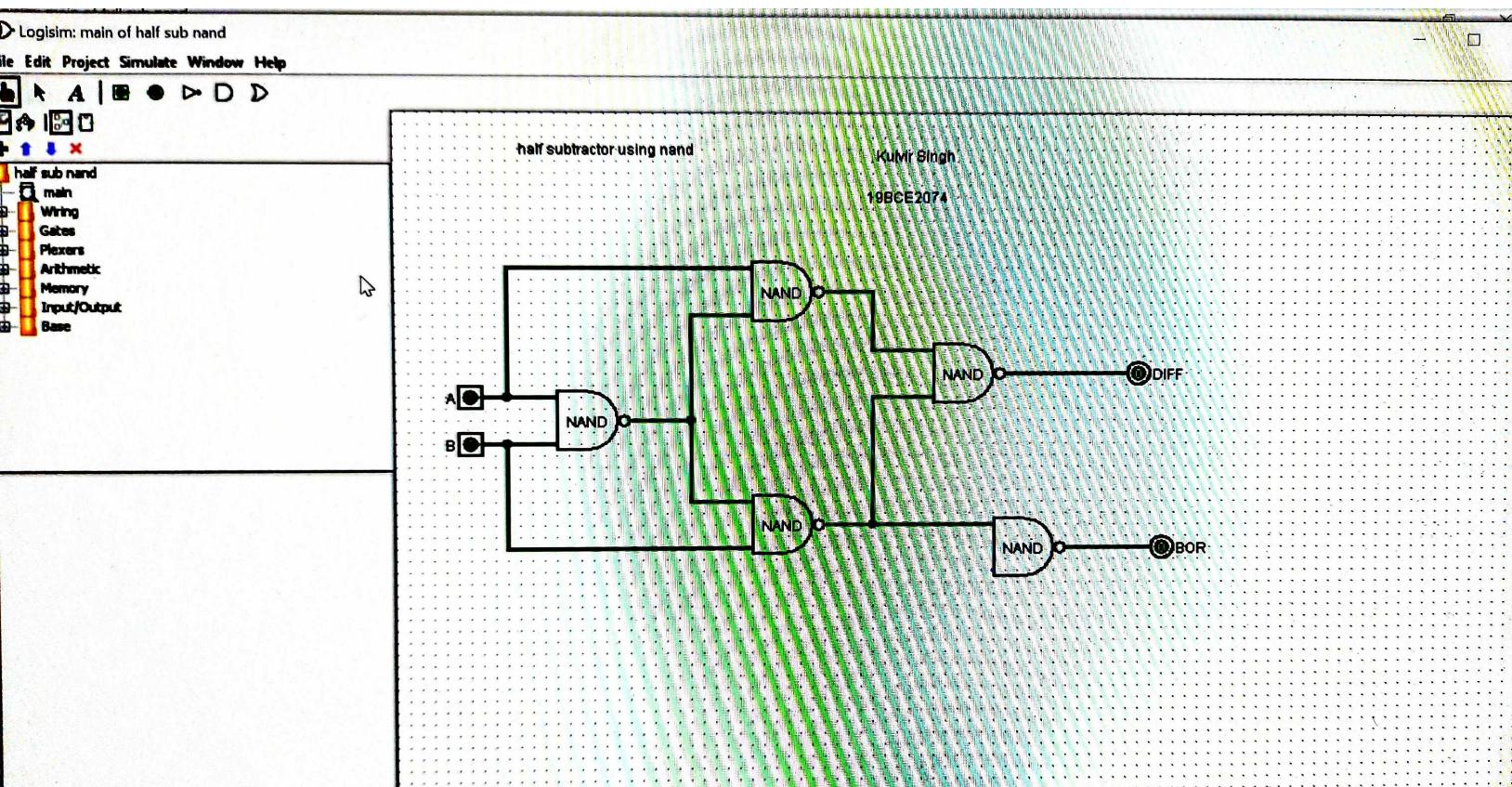


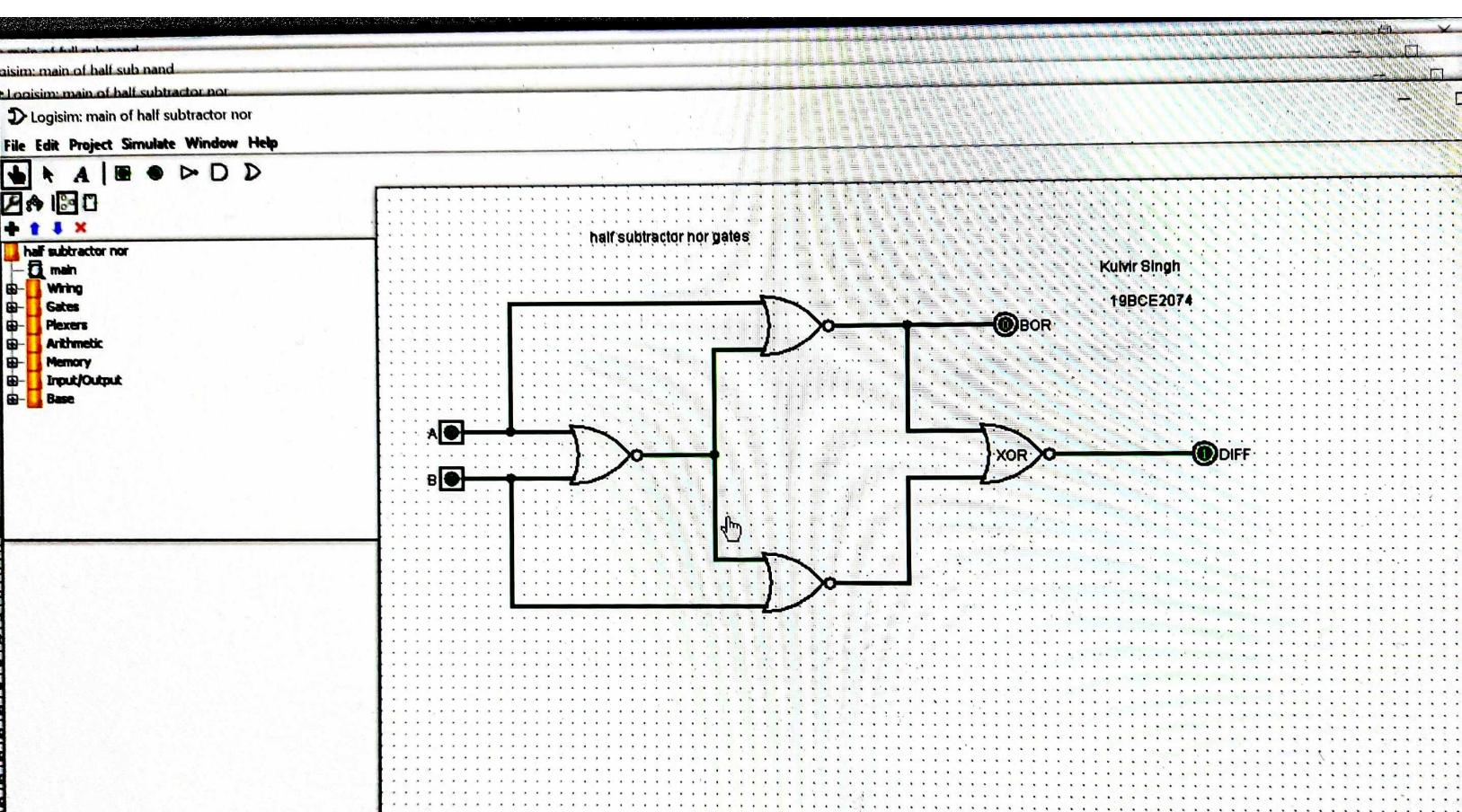


Truth Table.


| A | B | DIFF | BOR |
|---|---|------|-----|
| 0 | 0 | 00 | 0 |
| 0 | 1 | 00 | 1 |
| 1 | 0 | 11 | 0 |
| 1 | 1 | 10 | 0 |


Full Subtractor using NAND

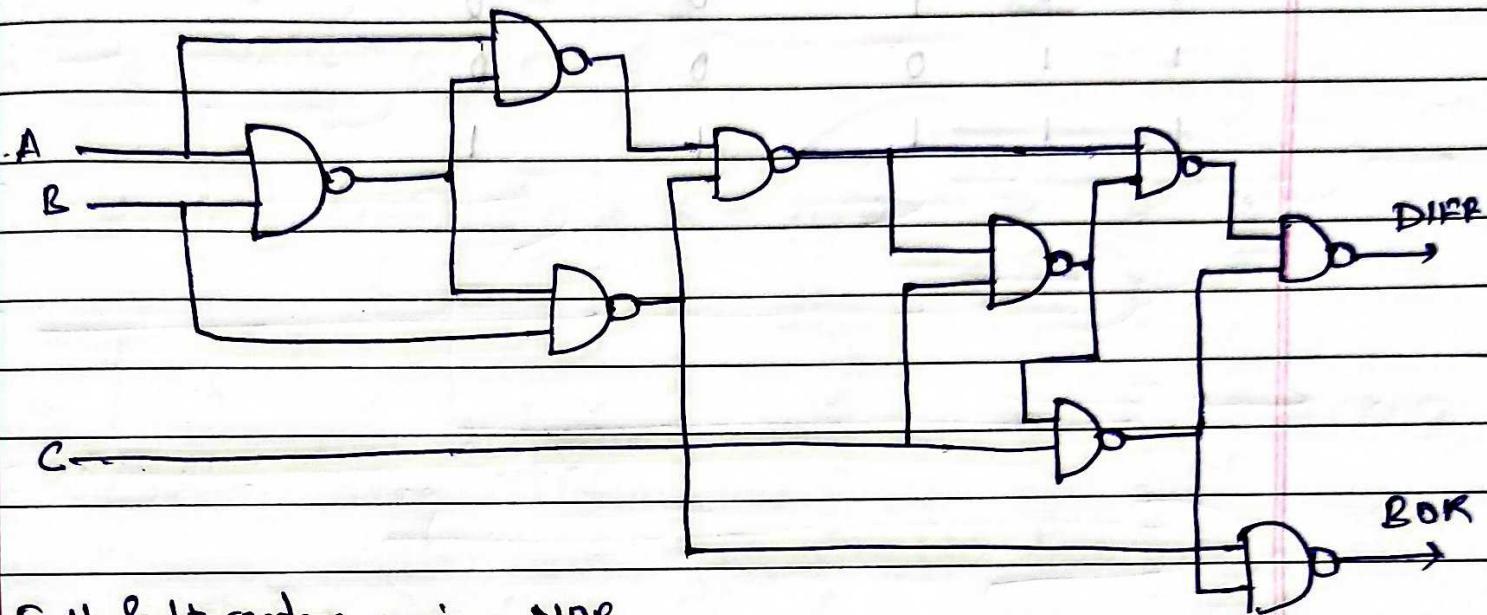

full Subtractor using NOR

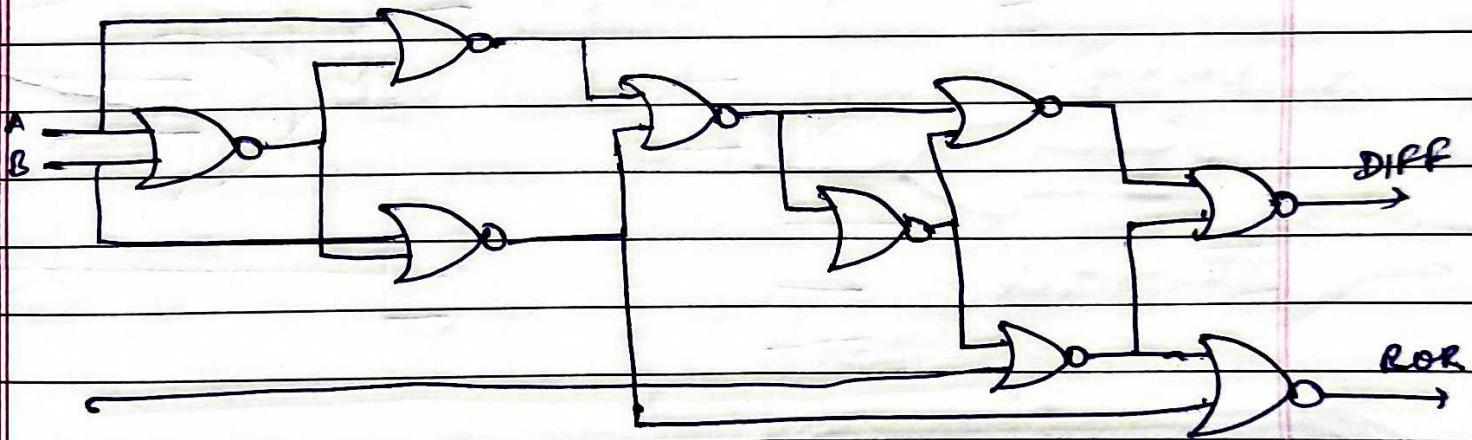

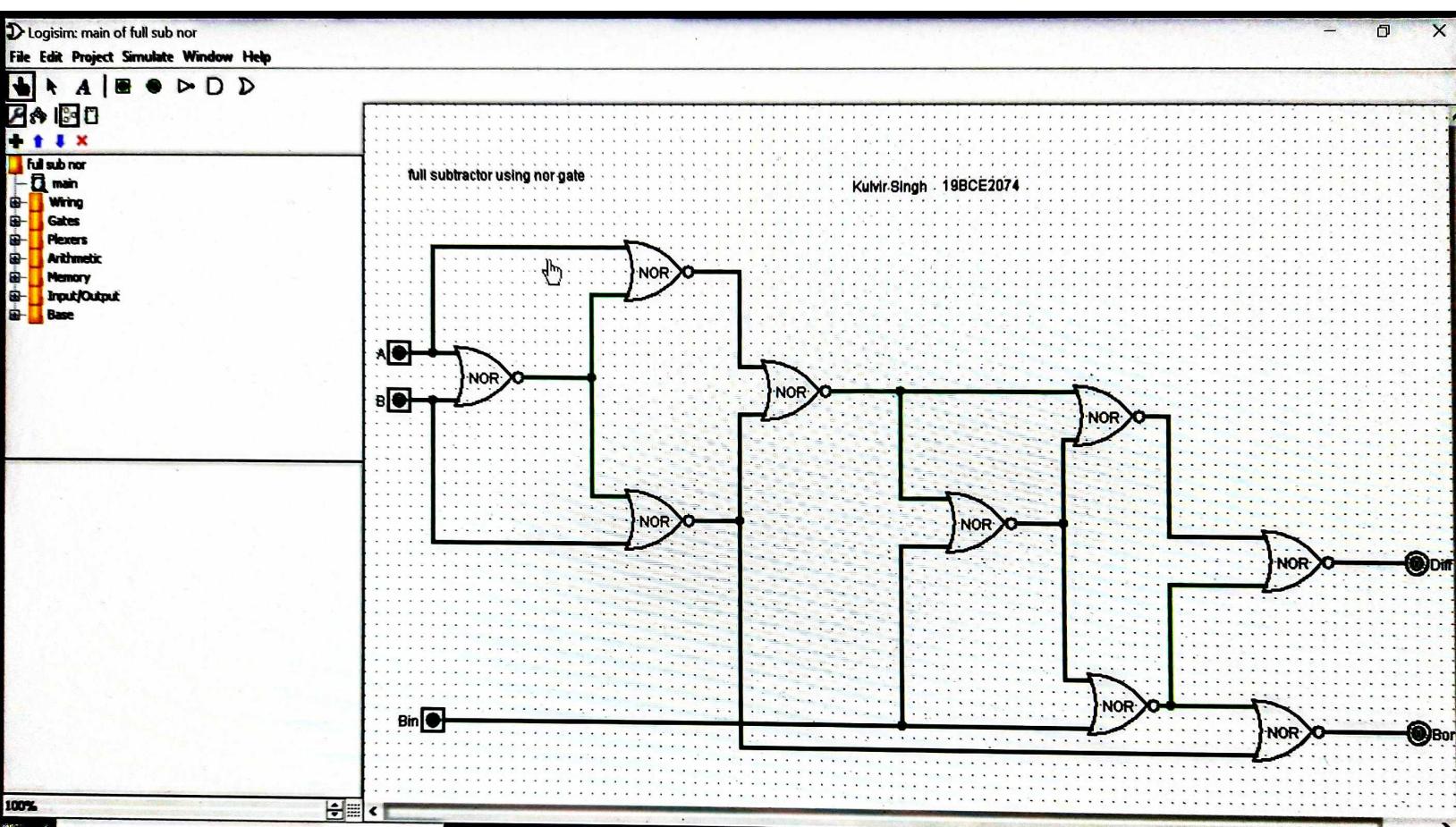

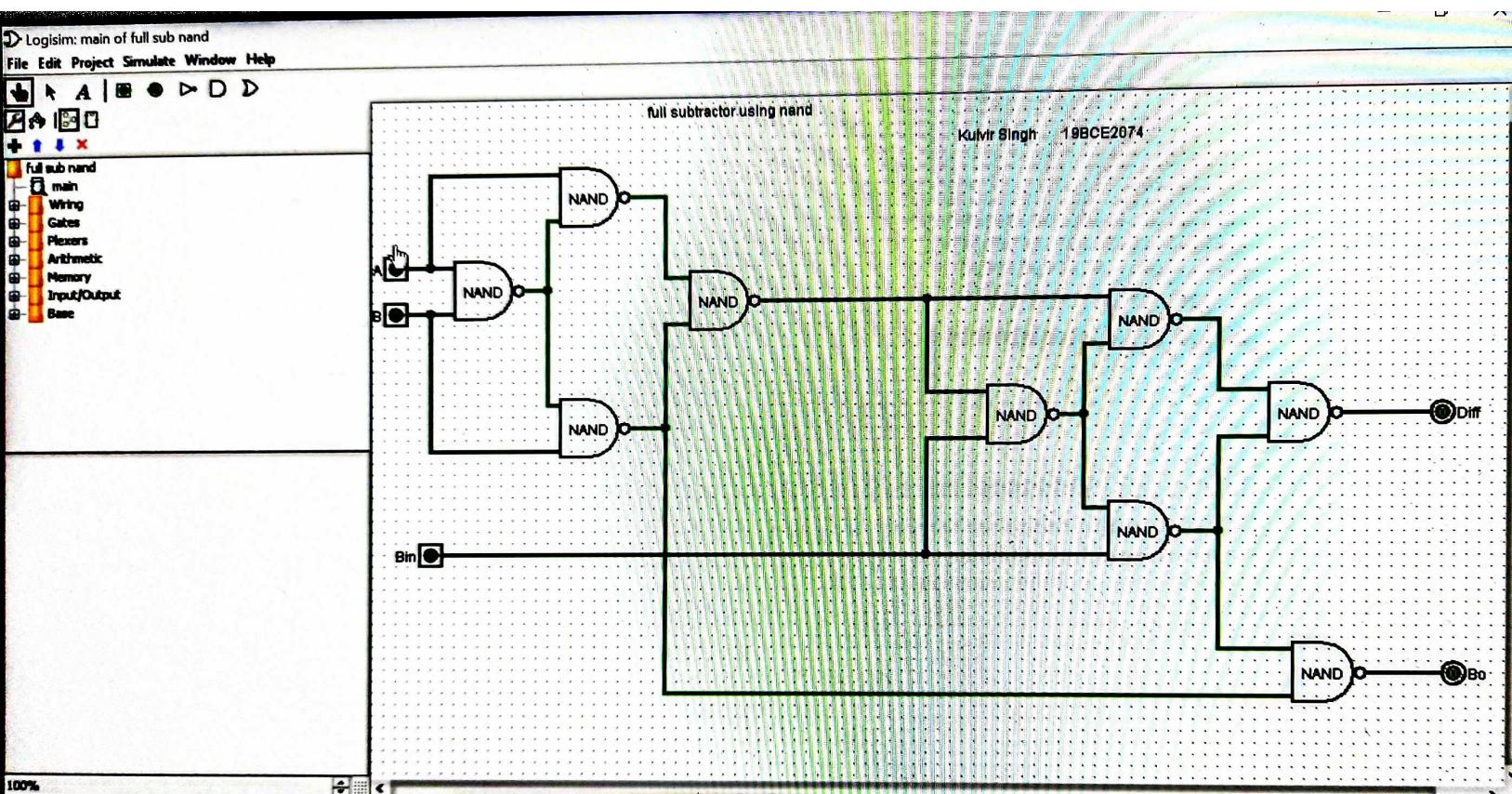

Truth Table

| A | B | C | D | DIFF | BOE |
|---|---|---|---|------|-----|
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 |