

Verification of KIRCHHOFF'S LAWS


(Mesh and Nodal Analysis)

Aim: To verify the Kirchhoff's current law and voltage law for the given network by theoretically and experimentally.

Apparatus/Tool required:

Sl. No.	Components Name	Range	Quantity
1	Resister	330Ω, 270Ω, 390Ω, 220Ω, 180Ω	Each 1 No.
2	Ammeter	0-50mA (DC)	1 No.
3	Voltmeter	0-30V (DC)	1 No.
4	RPS	0-32 V (DC)	1 No.
5	Connecting Wires	-	Few
6	Bread Board	-	1 No.

Circuit Diagram:

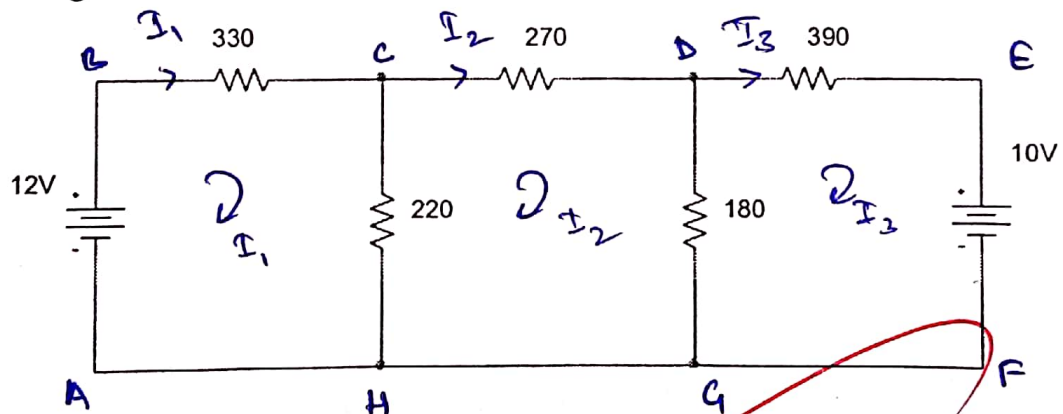

Theory:

Kirchhoff's Current Law (KCL): The algebraic sum of the current at any junction is zero.

$$\sum I = 0$$

Kirchhoff's Voltage Law (KVL): The algebraic sum of the voltage will be zero at any closed loop.

$$\sum V = 0$$

Mannual Practical Circuit and output:

Mesh Analysis:

ABCHA - (i)

$$12 - 330 I_1 - 220 (I_1 - I_2) = 0$$

$$12 - 330 I_1 - 220 I_1 + 220 I_2 = 0$$

$$12 - 550 I_1 + 220 I_2 = 0$$

$$\boxed{550 I_1 - 220 I_2 = 12} \quad \text{--- (1)}$$

KDCHC - (ii)

$$-270 I_2 - 180 (I_2 - I_3) - 220 (I_2 - I_1) = 0$$

$$-270 I_2 - 180 I_2 + 180 I_3 - 220 I_2 + 220 I_1 = 0$$

$$\boxed{220 I_1 - 670 I_2 + 180 I_3 = 0} \quad \text{--- (2)}$$


DEFCD - (iii)

$$-340 I_3 - 10 - 180 (I_3 - I_2) = 0$$

$$-340 I_3 - 10 - 180 I_3 + 180 I_2 = 0$$

KVL Proof 1
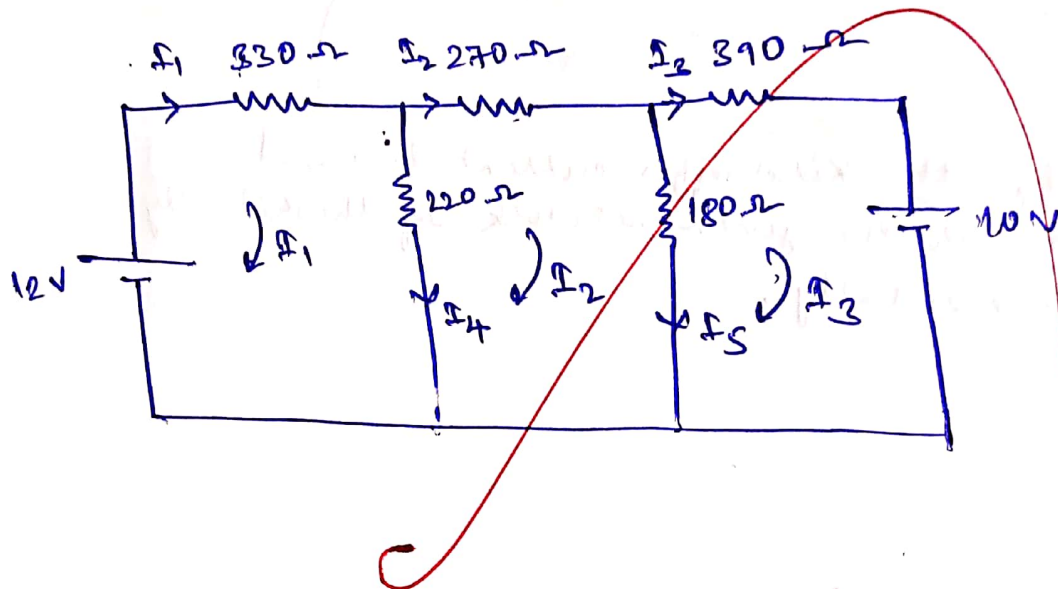
$$550 \times 23.06 \times 10^{-3} - 220 \times 3.12 \times 10^{-3} = 12$$



Practical Manual Calculations:

ABCHH - I


Mesh Analysis

$$12 - 330 I_1 - 220 (I_1 - I_2) = 0$$

$$12 - 330 I_1 - 220 I_1 + 220 I_2 = 0$$

$$\boxed{550 I_1 - 220 I_2 = 12}$$


CDHCH - II

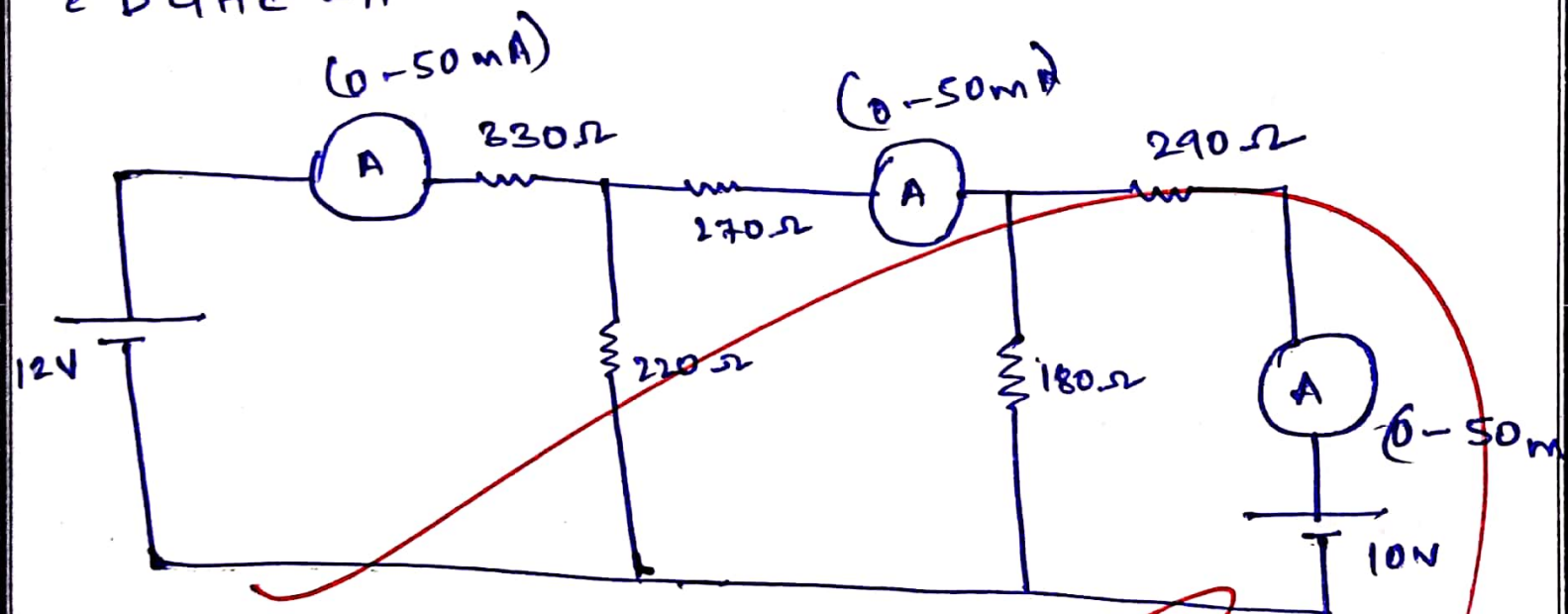


I_1 (mA)	23
I_2 (mA)	3
I_3 (mA)	16
$I_1 - I_2 = I_4$ (mA)	20

Practical Circuit and output:

Node Analysis:

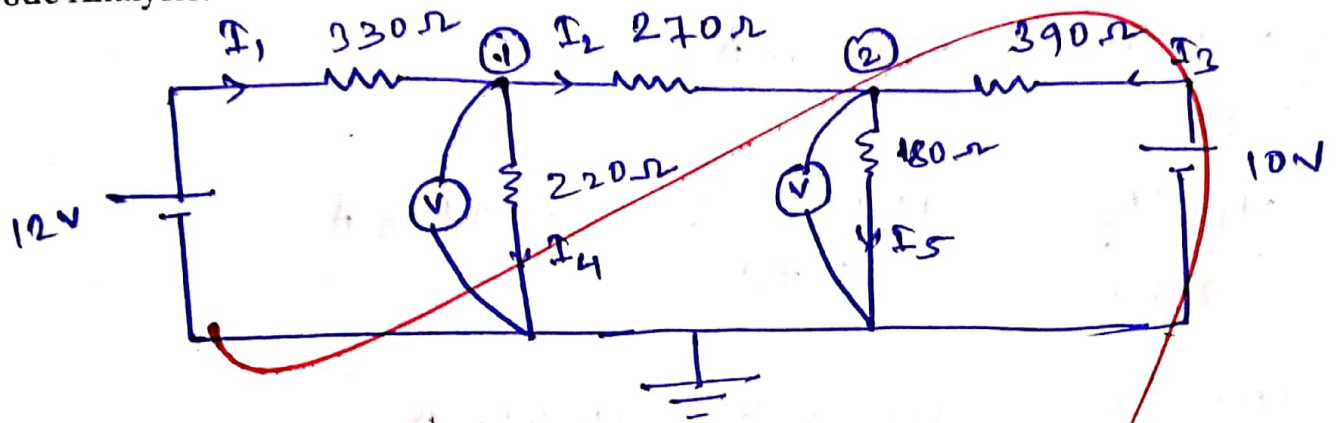

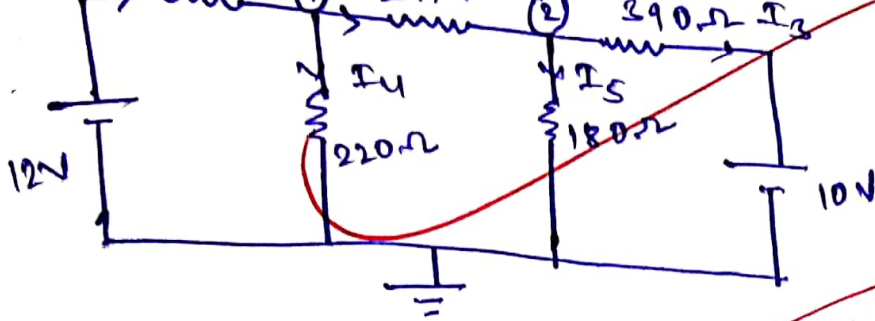

At node (1)

$$I_1 = I_2 + I_4 \quad \text{--- (i)}$$

$$I_1 = \frac{12 - V_1}{330} \quad \text{--- (ii)} \quad , \quad I_2 = \frac{V_1 - V_2}{270} \quad \text{--- (iii)} \quad , \quad I_4 = \frac{V_1 - 0}{220}$$

$$\Rightarrow \frac{12 - V_1}{330} = \frac{V_1 - V_2}{270} + \frac{V_1}{220}$$

$$\Rightarrow \frac{12}{330} - \frac{V_1}{330} - \frac{V_1}{270} + \frac{V_2}{270} - \frac{V_1}{220} = 0$$

$$\Rightarrow \frac{12}{330} - V_1 \left(\frac{1}{330} + \frac{1}{270} + \frac{1}{220} \right) + \frac{V_2}{270} = 0$$

$$\Rightarrow \boxed{-0.01127V_1 + 0.0037V_2 = -0.0364} \quad \text{--- (iv)}$$

At node (2) :

$$I_3 + I_2 = I_5 \quad \text{--- (v)}$$

$$I_3 = \frac{10 - V_2}{390} \quad \text{--- (vi)} \quad , \quad I_2 = \frac{V_1 - V_2}{270} \quad \text{--- (vii)} \quad , \quad I_5 = \frac{V_2 - 0}{180}$$

$$2) \frac{10 - V_2}{390} + \frac{V_1 - V_2}{270} = \frac{V_2}{180}$$

$$3) \frac{10}{390} - \frac{V_2}{390} + \frac{V_1}{270} - \frac{V_2}{270} - \frac{V_2}{180} = 0$$

$$\Rightarrow \frac{V_1}{270} - V_2 \left(\frac{1}{390} + \frac{1}{270} + \frac{1}{180} \right) + \frac{10}{390} = 0$$

$$\Rightarrow 0.0037 V_1 - 0.01182 V_2 = -0.0256$$

$$I_1 = \frac{12 - 4.4}{330} = 28.03 \text{ mA}$$

$$I_2 = \frac{V_1 - V_2}{270} = \frac{4.4 - 3.6}{270} = 2.96 \text{ mA}$$

$$I_3 = \frac{10 - V_2}{390} = \frac{10 - 3.6}{390} = 16.41 \text{ mA}$$

$$I_4 = \frac{4.4}{220} = 20 \text{ mA}$$

$$I_5 = \frac{3.6}{180} = 20 \text{ mA}$$

Procedure:

Result: The verification of KCL and KVL has been verified for the given network by theoretically and experimentally and the following results are tabulated;

Manual Calculations

Practical output

Parameters

Theoretical Value (mA)

Exp. Value (mA)

I_1

23.06

23

I_2

3.12

3

I_3

-16.56

-16

Node Voltage Analysis:

Manual Calculations

Practical output

Parameters

Theoretical Value (V)

Exp. Val. (V)

V_1

4.4

4.3

V_2

3.6

2.5

Inference:

Reg. No: 19BCE2074

Name: KULVIR SINGH

Date: 25.07.19